

Q1) (6 points) Find and sketch  $v_o(t)$  for the circuit of figure 1 mark all voltages clearly, given that  $V_{D1} = V_{D2} = 0.7V$  and  $v_i(t) = 10\sin\omega t$ , V.

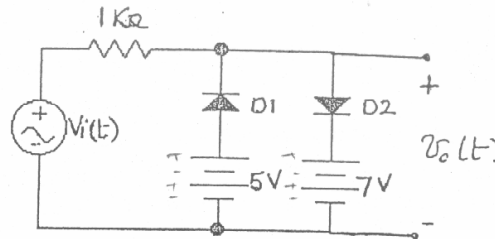


Figure 1

Q2) (10 points) For the circuit of figure 2, given that:

$$i_D(t) = \begin{cases} 2.5 \times 10^{-3} (v_D - 0.5)^2, & v_D \geq 0.5 \\ 0, & v_D \leq 0.5 \end{cases}$$

- Find and sketch the DC and AC load line equations.
- Find the total load voltage  $v_L(t)$ .

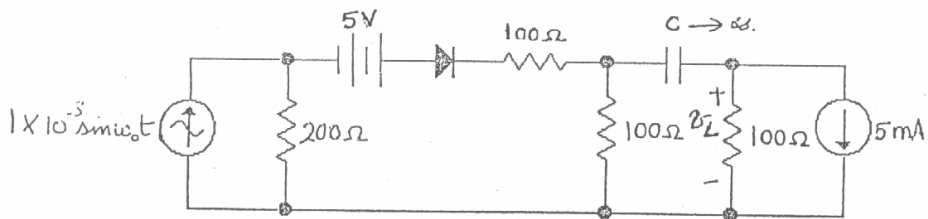


Figure 2

Q3) (9 points) For the transistor circuit of figure 3, given that  $V_{BEQ} = 0.7V$  and  $\alpha = 0.99$ .

- Find  $I_{BQ}$ ,  $I_{CQ}$ ,  $V_{CEQ}$ .
- Find and plot the DC load line equation.
- What is the maximum allowed peak to peak collector current swing?

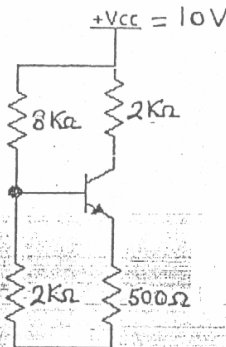


Figure 3