

EE210 - Electric Circuits I  
Exam I, Form: **B**

Name: \_\_\_\_\_

Student Numt \_\_\_\_\_

Section: \_\_\_\_\_


Date: 2007/10/30

The exam contains 2 parts: matching phrases, and short answer.

Total number of points in this exam = 100

Section 1. Short Answers-B-90 points

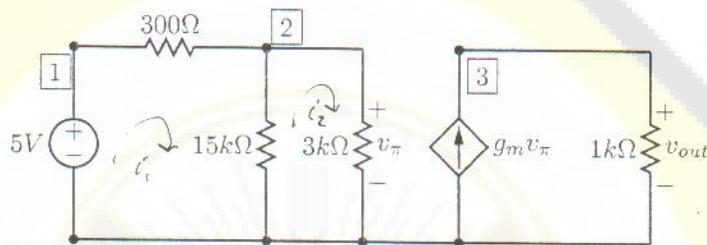1. **15 Points** In the circuit below, if  $g_m = 0.038$ , compute  $v_{out}$ .



use mesh analysis :-

$$\begin{aligned}
 -5 + 300i_1 + 15 \times 10^3(i_1 - i_2) &= 0 \Rightarrow 315i_1 - 15i_2 = 5 \Rightarrow i_2 = 0.0137 \text{ A} \\
 15 \times 10^3(i_2 - i_1) + 3 \times 10^3 i_2 &= 0 \Rightarrow -15i_1 + 18i_2 = 0
 \end{aligned}$$

-3


$$\begin{aligned}
 v_{out} &= \frac{I}{R} = \frac{g_m v_{\pi}}{1 \times 10^3} = \frac{0.038 \times 41.1}{1 \times 10^3} = 1.56 \times 10^{-3} \text{ V} \\
 &= I R = g_m v_{\pi} R = 0.038 \times 41.1 \times 1 \times 10^3 = 1561.8 \text{ V} \\
 &= 169.64 \text{ V}
 \end{aligned}$$

$v_{\pi} = 3 \times 10^3 \times 0.0137 = 4.11 \text{ V}$

2. **15 Points** For the circuit shown below,

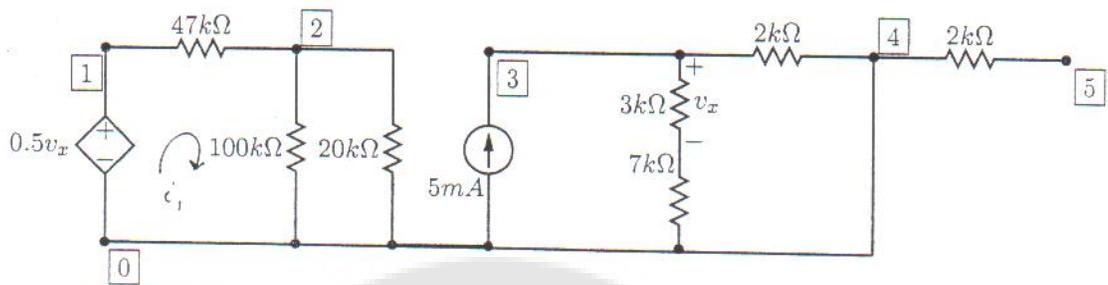- (a) what is the power dissipated by the 47 kΩ resistor ?
- (b) what is the voltage at node 5? zero volt





(a) Loop (1) and take  $\frac{1}{R_{eq}} = \frac{1}{100} + \frac{1}{20} \Rightarrow R_{eq} = \frac{50}{3}$

$$-0.5v_x + 47i_1 + \frac{50}{3}i_1 = 0$$

$$i_1 = \frac{0.5v_x}{63.66k\Omega}$$

V at node 5: ~~0~~

V at node 5 = 0

$$v_x = IR = 5 \times 10^{-3} \times 3 \times 10^3 = 15V$$

(-4)

$$\therefore i_1 = 0.1178A$$

$$\therefore P_{47\Omega} = i_1^2 R = 652.36W$$

(absorb +652.36W)

3. [15 Points] Determine each mesh current in the circuit shown below  $i_1$ ,  $i_2$ , and  $i_3$ .

$$v_x = i_1$$

mesh (1)

$$-6 + 5i_1 + i_1 - 2 = 0$$

$$6i_1 = 8 \Rightarrow i_1 = 1.33A$$

mesh (2)

$$i_2 = 0.1v_x \Rightarrow 0.133A$$


mesh (3)

$$2 + 12(i_3 - i_2) - 1.5 + 3i_3 = 0$$


$$2 + 12(i_3 - 0.133) - 1.5 + 3i_3 = 0$$

$$15i_3 = -0.5 + 1.596$$

$$i_3 = 0.073A$$

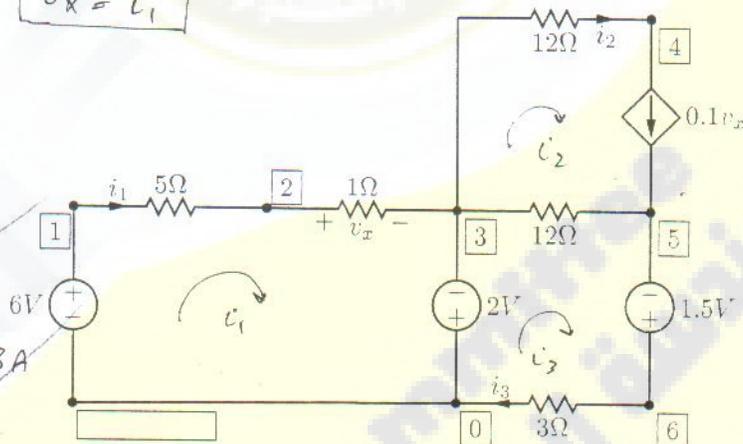

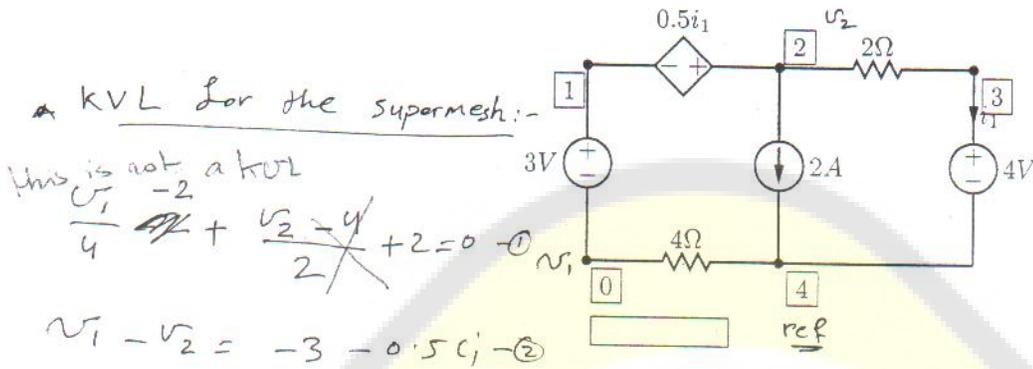4. **10 Points** Find  $i_1$  in the circuit shown below. *hint: write KVL for the supermesh*



KVL for the supermesh:-

*This is not a KVL*

$$\frac{v_1}{4} + \frac{v_2 - 4}{2} + 2 = 0 \quad \text{--- (1)}$$

$$v_1 - v_2 = -3 - 0.5i_1 \quad \text{--- (2)}$$

$$i_1 = \frac{v_2 - 4}{2}$$

$$\Rightarrow i_1 = \frac{3.63 - 4}{2} = -0.185 \text{ A}$$

$$\therefore \text{eq 2} \rightarrow v_1 - v_2 = -3 - 0.5 \left( \frac{v_2 - 4}{2} \right)$$

$$v_1 - v_2 + \frac{v_2}{4} = -3 + 1 \quad \text{--- (3)}$$


$$v_1 = \frac{3}{4}v_2 = -2$$

$$0.25v_1 + 0.5v_2 = 2$$

$$v_1 = 0.72$$

$$v_2 = 3.63$$

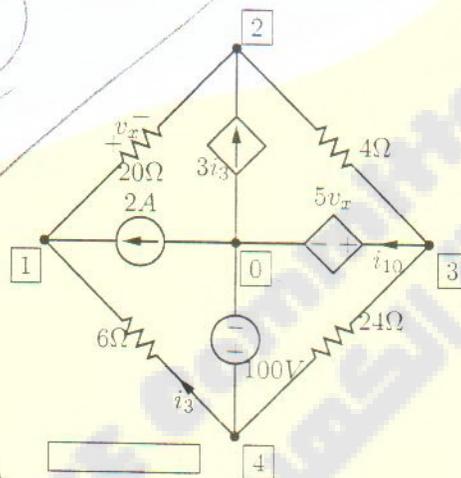
5. **15 Points** Determine the two currents labeled  $i_3$  and  $i_{10}$  in the circuit below.



(15)



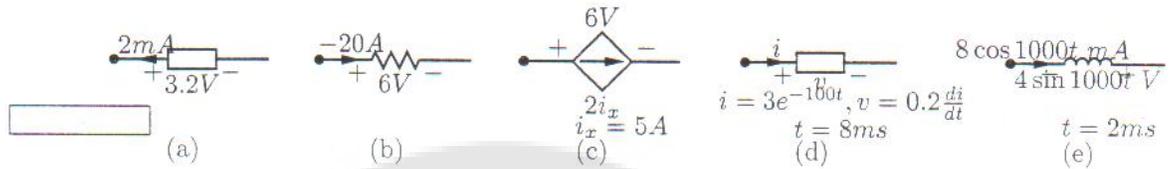6. 10 Points Determine the power being absorbed by each of the circuit elements shown in the figure below



(a)  $P = iV = (-2 \times 10^{-3} \times 3.2)$   
 $= -6.4 \times 10^{-3} \text{ W}$


(b)  $P = \frac{V^2}{R} = \frac{(6)^2}{6}$   
 $= iV = (-20)6 = -120 \text{ W}$

(c)  $P = iV = 2 \times 5 \times 6 = 60 \text{ W}$

(d)  $iV = 1.347 \times -26.95 = -36.31 \text{ W}$

(e)  $iV = (8 \cos 1000 \times 2 \times 10^{-3}) \times 10^{-3} \times 4 \sin 1000 \times 10^{-3}$   
 $= 1.16 \times 10^{-3} \text{ W}$

7. 10 Points For the circuit shown below, if  $v_2 = 1000i_2$  and  $i_2 = 5 \text{ mA}$ , determine  $v_s$ .

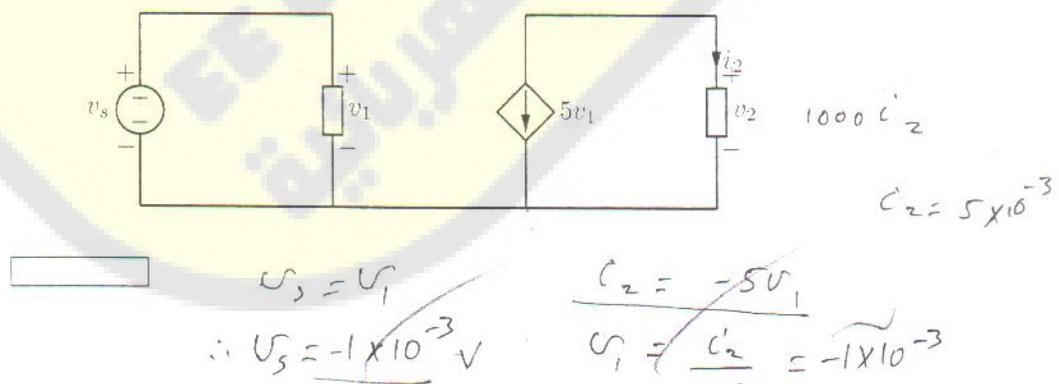

Section 2. 10 Points-B - 1 point each Match the corresponding phrases

- |                       |   |   |
|-----------------------|---|---|
| <del>f</del> <u>d</u> | KCL is a translation of the fact that               | <del>a</del> <u>voltages as the unknowns</u>    |
| <del>f</del> <u>f</u> | The unit for measuring energy is                    | (b) <i>common node</i>                          |
| <del>f</del> <u>A</u> | The unit for measuring power is                     | (c) <i>any circuit</i>                          |
| <del>f</del> <u>e</u> | Writing mesh equations applies to                   | (d) <i>currents as the unknowns</i>             |
| <del>f</del> <u>d</u> | Mesh equations have the                             | (e) <i>planar circuits</i>                      |
| <del>f</del> <u>a</u> | KVL is a translation of the law that                | (f) <i>Joule</i>                                |
| <del>f</del> <u>b</u> | Writing node equations applies to                   | (g) <i>energy is conserved</i>                  |
| <del>f</del> <u>a</u> | Nodal equations have the                            | (h) <i>number of mesh currents</i>              |
| <del>f</del> <u>j</u> | In using nodal analysis we do not write KCL for the | (i) <i>Watt</i>                                 |
| <del>f</del> <u>h</u> | Number of Mesh equations equals                     | <del>j</del> <u>a point can not hold charge</u> |

(-6)

EE Committee  
لجنة الهندسة الكهربائية



Name: \_\_\_\_\_  
Student Number: \_\_\_\_\_  
Section: \_\_\_\_\_  
Date: \_\_\_\_\_

The exam contains 2 parts: True/False and short answers.

Total number of points in this exam = 100

20 Points-B - 1 point each

Section 1.  
True/False

**True** The voltage across the capacitor can not change in zero-time interval.

**False** The two curves represent different sinusoids having the same frequency. The dotted curve represents a voltage that is leading the voltage represented by the solid curve.

**True** The capacitor can store finite amount of energy in its electric field only if the current passing through it is time-varying (not DC).

**False** The Norton equivalent circuit is simply a resistor connected in parallel with an independent voltage source.

**False** The inductor is open circuit for DC voltage.

**False** Maximum power transfer to a given load can be satisfied for any value of the load resistor.

**True** In a series RL circuit, the resistor voltage is proportional to the derivative of the inductor current.

**True** To apply superposition principle, the circuit should be linear.

**False** The load resistor absorbs maximum power if its value is one-half the Thevenin equivalent resistor.

**False** The capacitor is open circuit for DC currents.


**True** The ideal capacitor does not dissipate energy but only stores it for finite time period.

**True** The Norton equivalent is a source transformation of the Thevenin equivalent.

**True** The elements having their voltages or currents controlling dependent sources should not be included in source transformation.

**False** The Thevenin equivalent of a linear circuit is a simple resistor connected in series with dependent source.

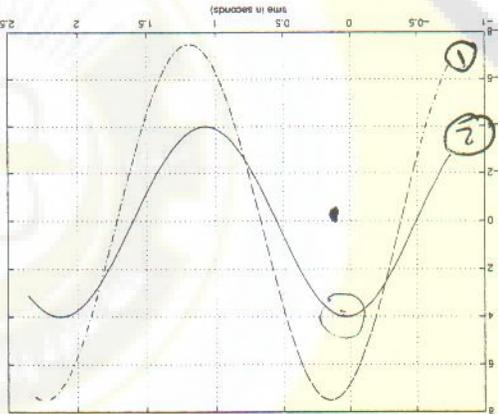**True** The Thevenin equivalent of a DC circuit that does not contain independent sources is a simple resistor.



② leads ①


17/20




Section 2. 80 points-B- 10 questions, 8 points each

5. The current through the capacitor is given by  $i(t)$ . If the energy stored at  $t = t_0$  is  $K J$ , what is the value of the capacitance? Take  $i(t) = 20 \sin(120t) A$ ,  $t_0 = 0.2 \text{ sec}$ ,  $K = 3$
6. If the current passing through an inductor  $i(t) = 4 + 5t^2$  and the voltage across it  $v_L(t) = 30t$  find  $L$  in Henry.
7. For the DC circuit shown below, find the voltage  $v_C$ . Take  $V_s = 12.5V$ ,  $R_1 = 2.5k\Omega$ ,  $R_2 = 20k\Omega$ ,  $C = 7\mu F$ .

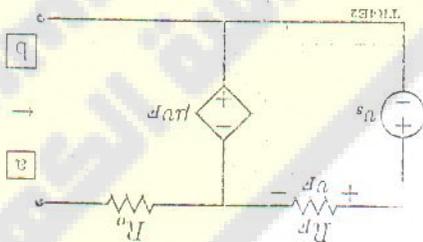
1. For the circuit shown below, Thevenin resistance  $R_T =$  as seen between  $a$  and  $b$  =



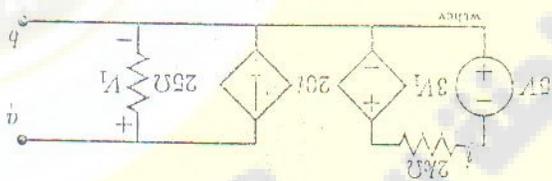
2. For the circuit shown below, find Thevenin equivalent circuit as seen between terminals  $a$  and  $b$ .



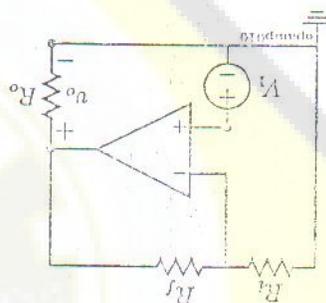
3. What value of  $R_f$  is required so that the power delivered to the  $R_o$  resistor is  $P_f$ ?  
Take  $R_1 = 150m\Omega$ ,  $R_f = 10k\Omega$ ,  $R_o = 10k\Omega$ ,  $V_1 = 10V$ .



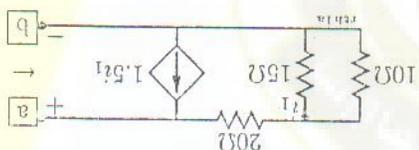
8. Find Thevenin's equivalent circuit voltage as seen between  $a$  and  $b$ .



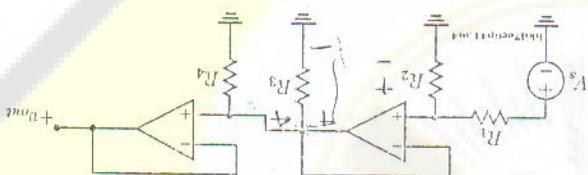9. Compute  $v_{out}$  for the two-stage opamp circuit below. Take  $V_s = 10V$ ,  $R_1 = 1k\Omega$ ,  $R_2 = 4k\Omega$ ,  $R_3 = 19k\Omega$ .



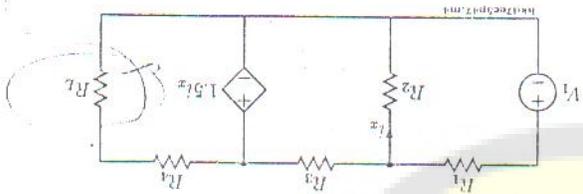10. (a) Find Thevenin equivalent of the network shown below as seen by the load resistor  $R_L$ .  
Take  $R_1 = 10\Omega$ ,  $R_2 = 20\Omega$ ,  $R_3 = 30\Omega$ ,  $R_4 = 40\Omega$ ,  $R_L = 10\Omega$ ,  $V_1 = 10$  Volts  
(b) Find the power dissipated in the load resistor  $R_L$ .



4. For the circuit shown below, compute the power dissipated by the resistors  $R_1$  and  $R_2$ . Take  $R_1 = 100\Omega$ ,  $R_2 = 200\Omega$ ,  $L = 1H$ ,  $V_s = 12V$ .

