


Name:

IU=

The exam has 5 questions for a total of 50 points.

Answer All Questions

1. [10pt] For the circuit shown below calculate the voltage
- v_{out}
- .

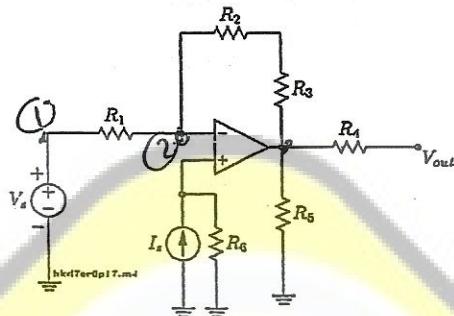Take $V_s = 5V$, $R_1 = 2k\Omega$, $R_2 = 10k\Omega$, $R_3 = 20k\Omega$, $R_4 = 200k\Omega$, $R_5 = 100k\Omega$, $R_6 = 2M\text{eg}\Omega$, $I_s = 1.5\mu\text{A}$.

$$V_p = 1.5 \text{ M} \times 2 \text{ meg}\Omega = 3 \text{ V} \quad \text{bcs } I_p = I_n = 0$$

$$V_n = V_p = 3$$

using Nodal Analysis at point (2)

$$\frac{(V_n - V_1)}{R_1} = \frac{(V_n - V_{out})}{R_2 + R_3} = 0$$

$$V_1 = V_s = 5V$$

$$\frac{(3 - 5)}{2k} - \frac{(3 - V_{out})}{30k} = 0$$

$$\frac{2}{2k} - \frac{3}{30k} - \frac{V_{out}}{30k} = 0$$

$$1 - 0.1 - \frac{V_{out}}{30k} = 0$$

$$0.9 - \frac{V_{out}}{30k} = 0$$

$$-2.7 \text{ V} = V_{out}$$

$$-2.7 \text{ V} = V_{out}$$

2. [10pt] A voltage $v(t) = \begin{cases} 5V & t < 0 \\ 5e^{-t/3}V, & t \geq 0 \end{cases}$ is applied to a $200\mu F$ capacitor.

- Compute the energy stored in the capacitor at $t = 3ms$.
- At what time has the energy stored in the capacitor dropped to 50% of its maximum value? (rounded to the nearest second)
- Determine the current flowing through the capacitor at $t = 1.5s$
- Calculate the power delivered by the capacitor to the external circuit at $t = 3s$

initial condition
 $V = 5V$

$$\begin{aligned} W &= \frac{1}{2} C \left(V(3ms)^2 - (5)^2 \right) \\ &= \frac{1}{2} \times 200 \times 10^{-6} \left(\left(5 e^{-\frac{(-3ms)}{3}} \right)^2 - 25 \right) \\ &= \frac{1}{2} \times 200 \times 10^{-6} (24.95 - 25) \\ &= -4.995 \times 10^{-6} \text{ J} \cdot V \end{aligned}$$

(b) $W_{max} \text{ at } t = 0$
thus
 $\frac{50}{100} \times \cancel{V^2}(25) = 5C$

$$12.5 = (5 e^{-t/3})^2$$

$$\frac{3.5355}{5} = \frac{5}{b} e^{-t/3}$$

$$\ln 0.70711 = -\frac{t}{3}$$

$$+0.3466 = +\frac{t}{3}$$

$$t = 1.04 \text{ second}$$

thus $t = 1 \text{ second}$ ✓

أولاً سلسلة المقاومات

مكعبات

C) current at $t = 1.5 \text{ s}$

$$\begin{aligned} i_C &= C \frac{dV_C}{dt} \\ &= 200 * 10^{-6} * \frac{-5}{3} e^{-t/3} \\ &= 200 * 10^{-6} * \frac{-5}{3} e^{-1.5/3} \\ &= 200 * 10^{-6} * \frac{-5}{3} e^{-\frac{1}{2}} \\ &= -2.022 * 10^{-7} \text{ A} \end{aligned}$$

d)


$$\begin{aligned} P_{\text{delivered to}} &= C V \frac{dV_C}{dt} = 200 * 10^{-6} * 5e^{-t/3} * \frac{5e^{-t/3}}{3} \\ &= 200 * 10^{-6} * 5e^{-1} * \frac{-5}{3} e^{-1} \\ &= -2.25558 * 10^{-4} \end{aligned}$$

thus power delivered by

$$= -P_{\text{delivered}}$$

thus $P_{\text{delivered}} = 2.25558 * 10^{-4} \text{ W}$

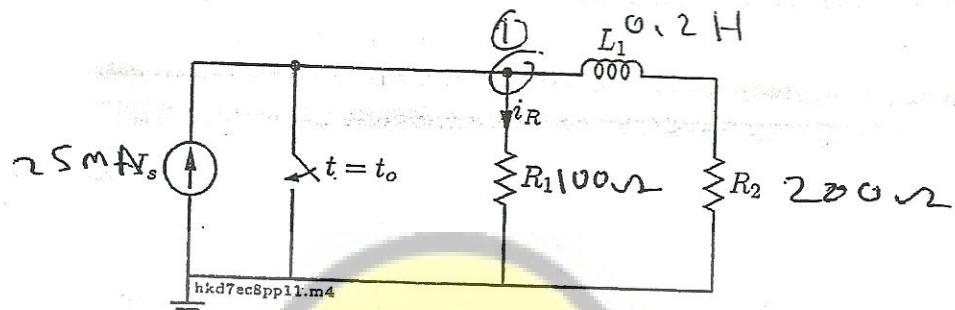3. [10pt] The circuit shown below has been in the form shown for a very long time. The switch opens at $t = t_0$.
 Take $t_0 = 3s$, $I_s = 25mA$, $R_1 = 100\Omega$, $L_1 = 0.2H$, $R_2 = 200\Omega$. Find i_R at (a) $t = 3^-$ (b) $t = 3^+$ (c) at $t = \infty$.



a) at $t = 3^-$

the switch was close thus it was short circuit

$$i_R = 0 \quad \checkmark \quad \text{no current pass through } i_R$$

$$\text{and } i_L = 0$$

b) at $t = 3^+$

the inductor not permitted suddenly change ϕ n. it's value of current thus at 3^+ like 3^-

$$i_L = 0A$$

taking V_C at node 1

$$+ 25m - i_R = 0$$

$$i_R = 25m \quad \checkmark$$

c) at $t = \infty$


the inductor be as short ckt bcs there is it's dc current

this

answ) elab is selig

سال ۱۵

۸

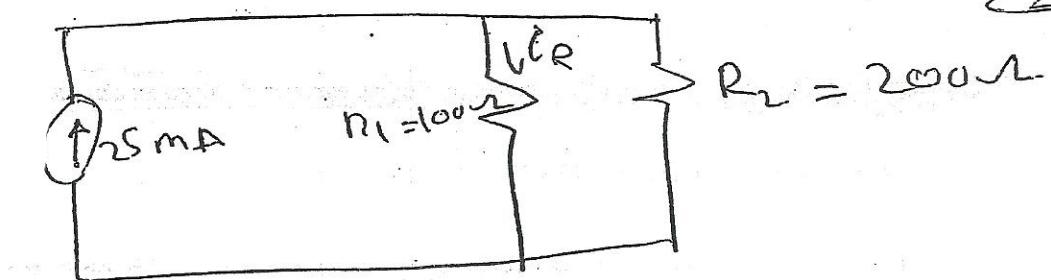

thus using current division


A hand-drawn diagram of a circular cross-section of a solenoid. The outer radius is labeled "25 mm" and the inner radius is labeled "100". Two resistors are shown in series: one with a value of $\frac{1}{100}$ and another with a value of $\frac{1}{200}$. The total current is labeled "0.01667 A".

4. [10pt] For the circuit shown below find the

- (a) open-circuit voltage V_{xy}
- (b) downward current in a short circuit between x and y
- (c) Thevenin equivalent impedance as seen from x and y

Take $v_s(t) = 2 \cos(1000t - 75^\circ) V$, $R_1 = 3\Omega$, $C_1 = 2 \text{ milli } F$, $R_2 = 12\Omega$, $L_1 = 15 \text{ milli } H$,

line domain

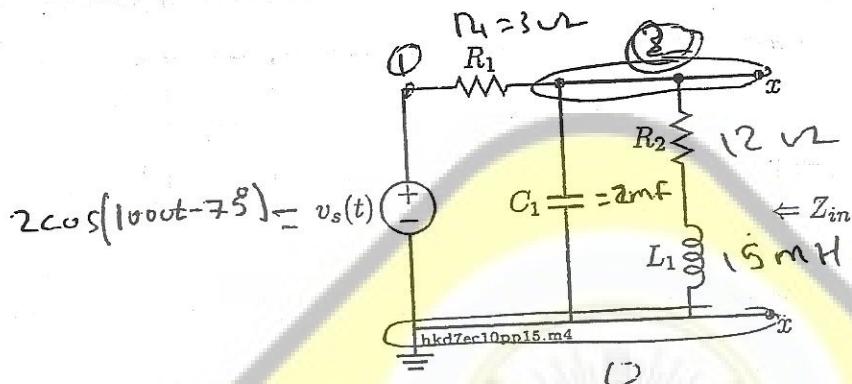

$$a). V_{xy} = V_{th}$$

using nodal analysis


$$w = 1000$$

$$L \text{ reactance} = JwL = j15m \times 1000 = j15\Omega$$

$$\text{C reactance} = \frac{-j}{wC} = \frac{-j}{1000 \times 2 \times 10^{-9}} = -j0.5\Omega$$

$$V_s(t) = 2 \angle -75^\circ$$

thus

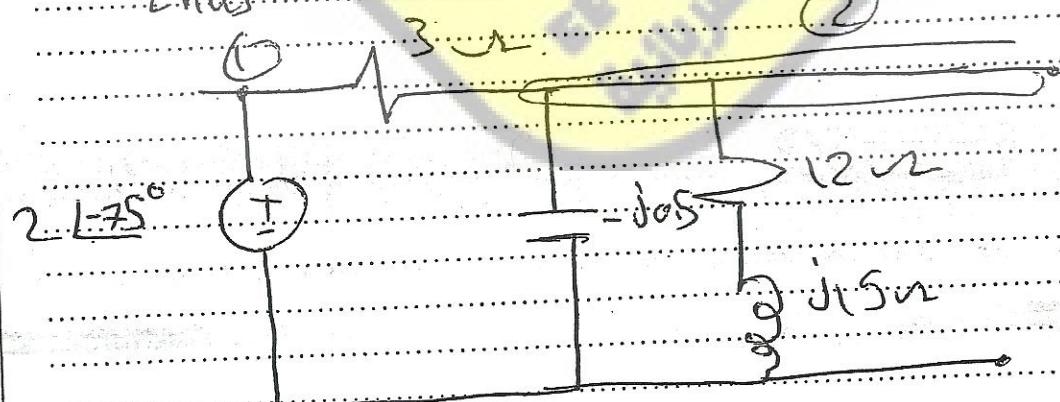

$$V_1 = 2 \angle -75^\circ$$

#

ANSWERED

$$V_1 = 2 \angle -75^\circ$$

$$\text{At } C1: - \left(\frac{V_2 - V_1}{3} \right) - \frac{V_2}{-j0.5} - \frac{V_2}{12+j15} = 0$$

$$- V_2 + \frac{V_1}{3} + \frac{V_2}{j0.5} - \frac{V_2}{12+j15} = 0$$


$$\left(-1 + \frac{1}{j0.5} - \frac{1}{12+j15} \right) V_2 = - \frac{V_1}{3}$$

$$\left(+1 - \frac{1}{j0.5} + \frac{1}{12+j15} \right) V_2 = \cancel{2} \frac{1}{3} \angle -75^\circ$$

$$V_2 = 0.3010 \angle -137.2^\circ$$

$$\text{thus } V_{xy} = 0.3010 \cos(100t - 137.2^\circ)$$

6)

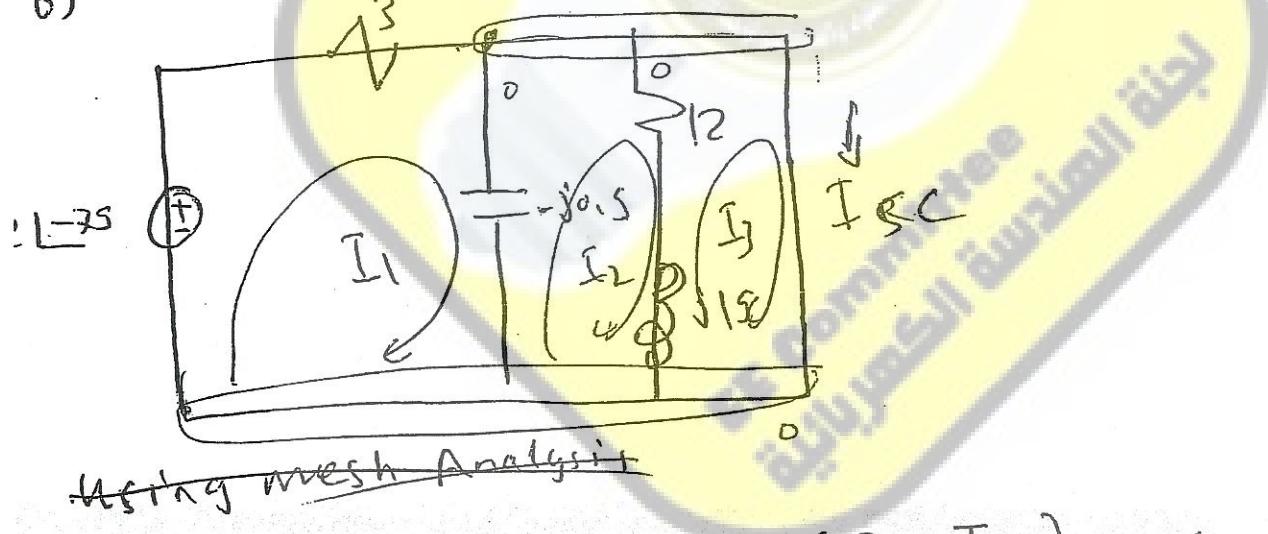

~~Using mesh Analysis~~

$$- \cancel{f_2 \angle 75^\circ} + 3I_1 - j0.9(I_1 - I_2) = 0$$

~~using nodal Analysis~~

$$-(V_2 - V_1) - I_{BC} = 0$$

$$+ \frac{V_1}{3} = I_{BC}$$

$$2 \angle -75^\circ = I_{BC}$$

$$I_{BC} = 2 \angle \frac{3}{3} \operatorname{cosec}(100\omega t - 75^\circ) A$$

~~Ics of short circuit~~

$$V_2 = 0$$

$$\text{thus } Z_{in} = \frac{V_{th}}{I_{sc}}$$


$$Z_{in} = \frac{0.301 \angle -137.2^\circ}{2 \angle -75^\circ}$$

$$Z_{in} = 0.4519 \angle -62.1^\circ$$

5. [10pt] Use PSpice to find the magnitude and phase of the current I_r and the real and imaginary of the voltage at node 4.

Take $v_s = 3 \cos(10^3 t - 37^\circ) V$, $R_1 = 100\Omega$, $C_1 = 100\mu F$, $C_2 = 300\mu F$, $L_1 = 0.5H$.

$$V_S = 3 \angle -37^\circ$$

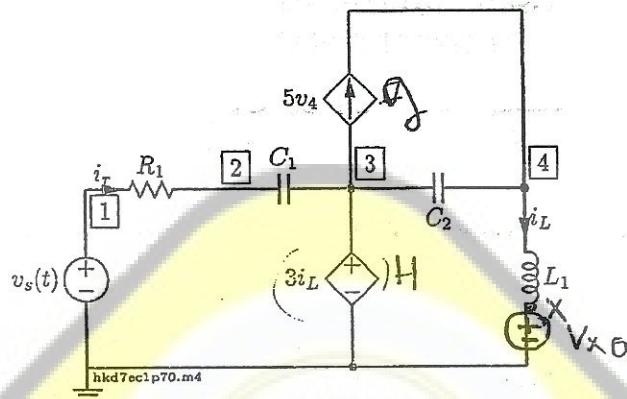

$$W = \frac{1000}{2\pi}$$

Title

```

VS 1 0 ac 3 -37
R1 1 2 100
C1 2 3 100u
C2 3 4 300u
L1 4 X 0.5
VXO X 0 ac 0 0
H1 3 0 VXO 3
g1 3 4 4 0 S
.ac Lin 1 1.5915 1.5915
.print ac im(VS) ip(VS)
.print ac vr(4) vi(4)
.end

```

(10)

