



Student Name:

Serial No.

Univ. No.

Section:

13. In the circuit of Figure (K), the initial values of  $di_L/dt$ , and  $dv_C/dt$  at  $t = 0^+$  are:

- |                                       |  |                                      |                                      |
|---------------------------------------|--|--------------------------------------|--------------------------------------|
| (a) $-8 \text{ A/s}, 50 \text{ kV/s}$ | (b) $-8 \text{ A/s}, -50 \text{ kV/s}$ | (c) $8 \text{ A/s}, -5 \text{ kV/s}$ | (d) $8 \text{ A/s}, 500 \text{ V/s}$ |
|---------------------------------------|--|--------------------------------------|--------------------------------------|

14. In the RLC circuit of Figure (L),  $i_L(0^-) = 0$ ,  $v_C(0^-) = 0$ , and  $t_1 > 0$ . Therefore, for  $0 < t < t_1$ , the form of the response  $v_C(t)$  in volts may be expressed as:

- |                             |  |
|-----------------------------|--|
| (a) $5 + (A + Bt)e^{-0.4t}$ | (b) $-5 + [5 \cos(1.936t) + B \sin(1.936t)]e^{-4t}$  |
| (c) $-5 + (A + Bt)e^{-4t}$  | (d) $5 + [A \cos(1.936t) + B \sin(1.936t)]e^{-0.4t}$ |

15. In the RLC circuit problem of Figure (L), for  $t > t_1$ , the form of the response  $v_C(t)$  in volts is:

- |                       |                                   |                       |                        |
|-----------------------|-----------------------------------|-----------------------|------------------------|
| (a) $(A + Bt)e^{-2t}$ | (b) $Ae^{-3.414t} + Be^{-0.586t}$ | (c) $Ae^{-2t} \cos t$ | (d) $Ae^{-2t} \sin 2t$ |
|-----------------------|-----------------------------------|-----------------------|------------------------|

16. In a critically damped parallel RLC circuit, the capacitor voltage response to a step-input current is as shown in Figure (M). This indicates that the value of  $\alpha$  is:

- |                        |                        |                       |                        |
|------------------------|------------------------|-----------------------|------------------------|
| (a) $200 \text{ Np/s}$ | (b) $100 \text{ Np/s}$ | (c) $47 \text{ Np/s}$ | (d) $150 \text{ Np/s}$ |
|------------------------|------------------------|-----------------------|------------------------|

17. In a series RLC circuit, the current response to a step-input voltage is as shown in Figure (N). This yields the following values for  $\alpha$  in Np/s,  $\omega_d$  and  $\omega_0$  in rad/s, respectively:

- |                       |                        |                        |                        |
|-----------------------|------------------------|------------------------|------------------------|
| (a) $100, 3248, 3250$ | (b) $2000, 3464, 4000$ | (c) $1000, 3142, 3297$ | (d) $2000, 3000, 3606$ |
|-----------------------|------------------------|------------------------|------------------------|

18. The sum,  $V_s$ , of the phasors  $V_1 = 13 \angle 22.62^\circ \text{ V}$ ,  $V_2 = 10 \angle 143.13^\circ \text{ V}$ , and  $V_3 = 5 \angle -53.13^\circ \text{ V}$  is:

- |  |   |   |  |
|--|---|---|--|
| (a) $V_s = 21.2 \angle 45^\circ \text{ V}$ | (b) $V_s = 9.9 \angle 45^\circ \text{ V}$ | (c) $V_s = 14.1 \angle -45^\circ \text{ V}$ | (d) $V_s = 11.4 \angle 37.9^\circ \text{ V}$ |
|--|---|---|--|

19. In the circuit of Figure (O), the value of  $L$  that makes  $i_g(t)$  in phase with  $v_g(t) = 80 \cos(5000t) \text{ V}$  is:

- |                   |                     |                                      |                                     |
|-------------------|---------------------|--------------------------------------|-------------------------------------|
| (a) $2 \text{ H}$ | (b) $0.5 \text{ H}$ | (c) $1 \text{ H or } 0.25 \text{ H}$ | (d) $2 \text{ H or } 0.5 \text{ H}$ |
|-------------------|---------------------|--------------------------------------|-------------------------------------|

20. When  $i_g(t)$  in the circuit problem of Figure (O) is in phase with  $v_g(t)$ , its peak value is:

- |                                    |                     |                                    |                     |
|------------------------------------|---------------------|------------------------------------|---------------------|
| (a) $80 \text{ or } 20 \text{ mA}$ | (b) $80 \text{ mA}$ | (c) $40 \text{ or } 20 \text{ mA}$ | (d) $20 \text{ mA}$ |
|------------------------------------|---------------------|------------------------------------|---------------------|

21. In the circuit of Figure (P),  $i_s(t) = 12.5 \cos(5000t) \text{ mA}$ . Therefore, the peak value of  $v_0(t)$  is:

- |                       |                      |                       |                       |
|-----------------------|----------------------|-----------------------|-----------------------|
| (a) $22.36 \text{ V}$ | (b) $67.1 \text{ V}$ | (c) $89.44 \text{ V}$ | (d) $44.72 \text{ V}$ |
|-----------------------|----------------------|-----------------------|-----------------------|

22. For the circuit of Figure (Q) with  $\omega = 1 \text{ rad/s}$ , the equivalent Thevenin voltage seen at x-y is:

- |                                       |  |  |                                       |
|---------------------------------------|--|--|---------------------------------------|
| (a) $1.414 \angle 45^\circ \text{ V}$ | (b) $0.707 \angle -90^\circ \text{ V}$ | (c) $0.707 \angle -45^\circ \text{ V}$ | (d) $1.414 \angle 90^\circ \text{ V}$ |
|---------------------------------------|--|--|---------------------------------------|

23. At  $f = 318.31 \text{ Hz}$ ,  $Z = 0.8944 \angle 26.57^\circ \Omega$  can be represented by two elements in parallel as:

- |   |   |   |   |
|---|---|---|---|
| (a) $R, L = 2 \text{ k}\Omega, 1 \text{ H}$ | (b) $R, C = 1 \text{ k}\Omega, 1 \mu\text{F}$ | (c) $R, C = 2 \text{ k}\Omega, 2 \mu\text{F}$ | (d) $R, L = 1 \text{ k}\Omega, 1 \text{ H}$ |
|---|---|---|---|

24. As a function of  $\omega$ , the imaginary part of the input impedance,  $Z_i$ , of the circuit of Figure (R) is:

- |                                       |   |
|---------------------------------------|---|
| (a) $100 \omega^2 / (\omega^2 + 100)$ | (b) $50 (\omega^2 - 100) / [\omega (\omega^2 + 100)]$ |
| (c) $100 \omega / (\omega^2 - 100)$   | (d) $50 (\omega^2 - 100) / (\omega^2 + 100)$          |

