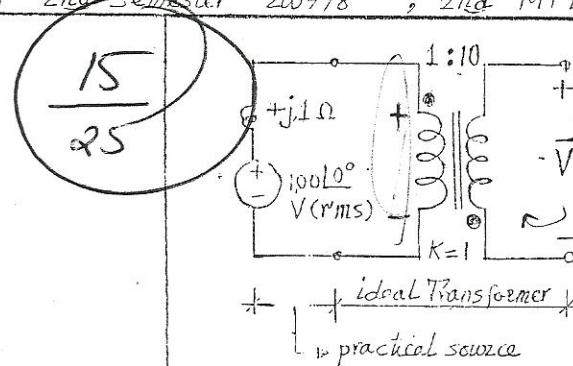


Q1 (D problem)

\bar{V} equals :


- a) $100 \angle 180^\circ$ V (rms)
- b) $10 \angle 0^\circ$ V (rms)
- c) $10 \angle -180^\circ$ V (rms)
- d) $1000 \angle 0^\circ$ V (rms)
- e) $1000 \angle 180^\circ$ V (rms)



Q2 (C problem)

The impedance seen by the source consists of:

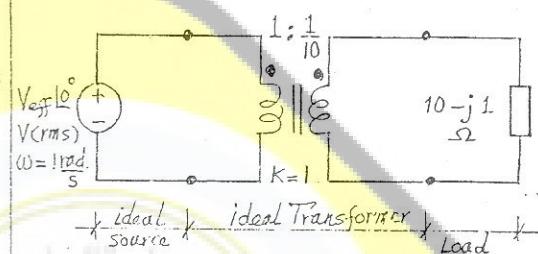
- a) $R = 1\Omega$ in series with $C = 10\text{mF}$
- b) $R = 0.1\Omega$ in series with $C = 100\text{F}$
- c) $R = 100\Omega$ in series with $C = 100\text{nF}$
- d) $R = 1\Omega$ in series with $C = 10\text{F}$
- e) $R = 1000\Omega$ in series with $L = 10\text{mH}$



Q3 (B problem)

\bar{V} equals :

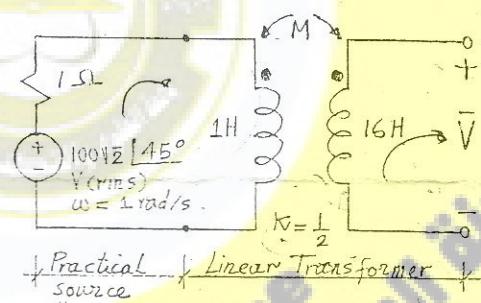
- a) $100\sqrt{2} \angle 90^\circ$ V (rms)
- b) $100 \angle 0^\circ$ V (rms)
- c) $200 \angle +90^\circ$ V (rms)
- d) $100 \angle +45^\circ$ V (rms)
- e) $200 \angle -45^\circ$ V (rms)



Q4 (B problem)

$V(t)$ equals :

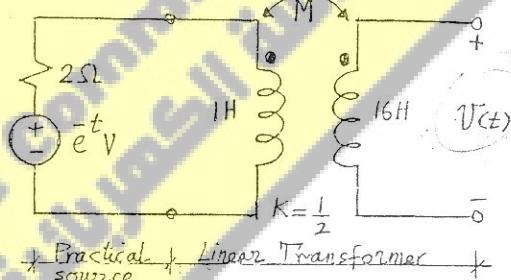
- a) $+4e^{+t}$ V
- b) $-2\bar{e}^{-t}$ V
- c) $+2e^{-t/2}$ V
- d) $+e^{-t}$ V
- e) $-e^{-t}$ V



Q5 (A problem)


The ratio \bar{I}_1 / \bar{I}_2 equals :

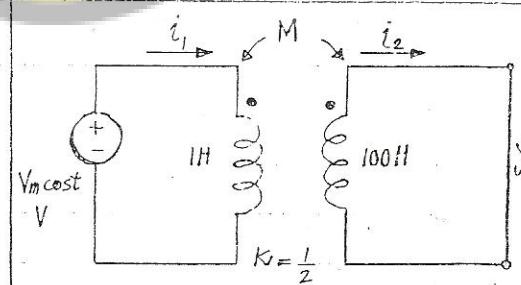- a) $10 \angle -30^\circ$
- b) $10 \angle 30^\circ$
- c) $20 \angle -90^\circ$
- d) $20 \angle 0^\circ$
- e) $20 \angle 90^\circ$




Q6) The Laplace transform of the voltage waveform shown is:

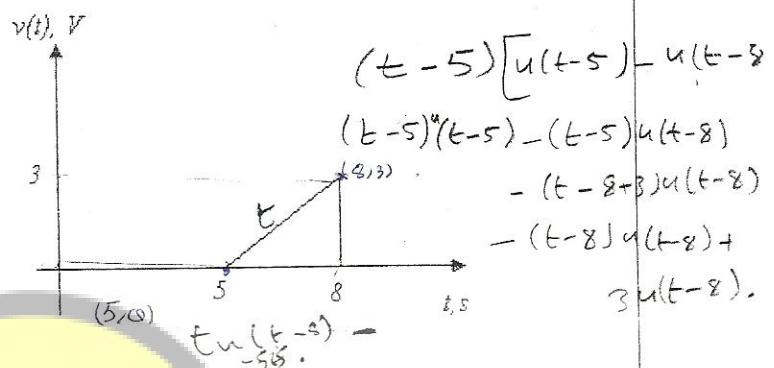- a. $V(s) = \frac{1}{s^2} (e^{-5s} - e^{-8s}) - \frac{3}{s} e^{-8s}$
- b. $V(s) = \frac{1}{s^2} (e^{-5s} - e^{-8s})$
- c. $V(s) = \frac{1}{s^2} (e^{5s} - e^{8s}) - \frac{3}{s} e^{8s}$
- d. $V(s) = \frac{1}{s^2} (e^{5s} - e^{8s})$



Q7) For the circuit shown $V(s)$ is:

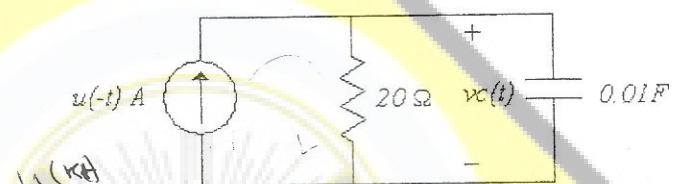- a. $\frac{100}{s(s+5)}$
- b. $\frac{-100}{s(s+5)}$
- c. $\frac{20}{s+5}$
- d. $\frac{-20}{s+5}$



$$\frac{3-\infty}{s-5} = \frac{3}{3} = 1$$

Q8) The inverse Laplace transform for $F(s) = \frac{1}{s^2(s+1)}$ is:

- a. $f(t) = te^{-t}u(t)$
- b. $f(t) = (1 + e^{-t})u(t)$
- c. $f(t) = (t + e^{-t})u(t)$
- d. $f(t) = (t - 1 + e^{-t})u(t)$


$$\frac{-1}{s} + 20$$

Q9) Given $F(s) = \frac{2s^3 - s^2 - 3s - 5}{s^3 + 6s^2 + 10s}$. $f(0^+)$, $f(\infty)$ respectively are:

- a. $-0.5, \infty$
- b. $\infty, -0.5$
- c. $-\infty, \infty$
- d. $0, \infty$

Q10) The s-domain circuit model shown represents:

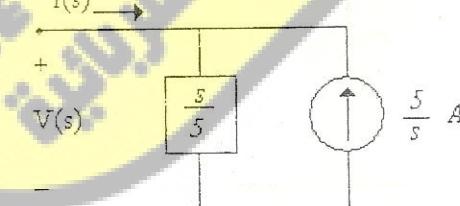- a. $C = 5F, v_c(0) = 5V$
- b. $C = 0.2F, v_c(0) = 0.2V$
- c. $L = 0.2H, i_L(0) = -5A$
- d. $L = 0.2H, i_L(0) = 5A$



Q	1	2	3	4	5	6	7	8	9	10
Ans.	<input checked="" type="radio"/> d	<input checked="" type="radio"/> a	<input checked="" type="radio"/> c	<input checked="" type="radio"/> b	<input checked="" type="radio"/> d	<input checked="" type="radio"/> a	<input checked="" type="radio"/> a	<input checked="" type="radio"/> b	<input checked="" type="radio"/> b	<input checked="" type="radio"/> d

$$(2s-13) + \frac{55s+125}{s^2+6s+10}$$

$$s^2 + 6s + 10$$

$$\frac{2s^3 - s^2 - 3s - 5}{s^2 + 6s + 10}$$

$$\frac{2s^3 + 6s^2 + 10}{s^2 + 6s + 10}$$

$$\frac{2s^3 - s^2 - 3s - 5}{s^2 + 6s + 10}$$

$$\frac{-13s^2 - 23s - 5}{s^2 + 6s + 10}$$

$$\frac{+13s^2 + 78s + 130}{s^2 + 6s + 10}$$

$$\frac{55s + 125}{s^2 + 6s + 10}$$

Jordan University of Science & Technology
Electrical Engineering Department
2nd Examination


EE214

Circuits II

29 Jul. 2008

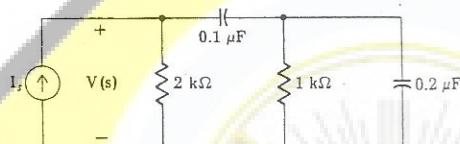
Q1 (10marks)

Find all the critical frequencies of the ratio $V(s)/I_s$, for the circuit shown, and sketch the magnitude of the ratio as a function of σ



Q2 (10marks)

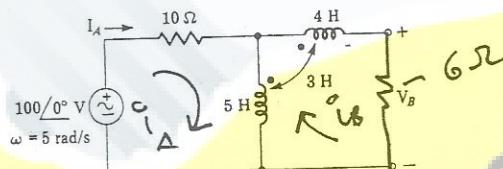- (a) Find I_A and V_B for the circuit illustrated in the following figure
- (b) Repeat if a 6Ω resistor is connected between the terminals at the right



Q3 (10marks)

Use several operational amplifiers in cascade to realize the transfer function $H(s) = V_{out} / V_{in} = 100 (s+100) / (s+1000)$