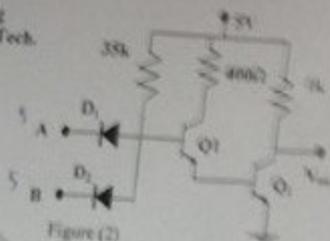


Answer all of the following questions

Question 1 (10 points)

For the following circuit shown in figure (2) if $\beta=50$, $V_D=0.7V$, $V_{BEA}=0.7V$,
 $V_{RES}=0.8V$, $V_{CES}=0.2V$



a) If $A=B=5V$, then find

$$V_{BE} = V_{BEA} + V_{BEF} = 0.7 + 0.8 = 1.5V$$

$$I_{B1} =$$

$$I_{C1} = \frac{5 - 1.5}{35k} = 1.116 \times 10^{-4} A$$

$$I_{B2} = \frac{5 - 0.2}{400} = 0.012$$

$$I_{B2} = I_{E1} = (\beta + 1) I_{B1} = (50 + 1) \times 1.116 \times 10^{-4} = 5.1 \times 10^{-4}$$

b) Find the Fan out of the gate if $I_{B2} = 1mA$

c) if $A=B=0.2V$, then $V_{out} =$

d) Find the noise margin of logic zero

$$NM_L = V_{IL} - V_{OL} = 0.7 - 0.2 = 0.5$$

and find the noise margin of logic one

$$NM_H = V_{OH} - V_{IH} = 5 - 0.8 = 4.2$$

Handwritten notes and calculations in red ink:

- 9, 7/10
- 9 ~ 8/10
- 8 ~ 2/10
- Large circled number 9

Question II (10 points)

For the following circuit shown in figure (3)

if $\beta = 50$, $\beta_1 = 0.2$, $V_D = 0.7V$, $V_{BEA} = 0.7V$, $V_{BE5} = 0.8V$, $V_{CES} = 0.2V$

a) If $A=B=$ Logic one and $I_{B3} = 2mA$ then find

- I_{E2}

$$V_E = 1.6 \Rightarrow I_{E2} = \frac{1.6}{2k} = 8 \times 10^{-4}$$

- V_{C2}

- I_{C2}

- I_{B2}

- R_X

b) If the Fan out the gate is 100 gates and $R_X = 2k\Omega$, find I_{B3}

c) If $A=B=$ Logic zero and $R_X = 2k\Omega$. If the gate is connected to 50 similar gates find

- I_{E4}

- V_{out}


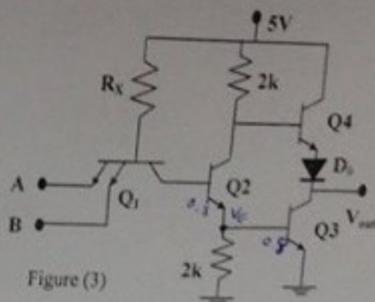


Figure (3)

LC Committee
لجنة الهندسة الكهربائية

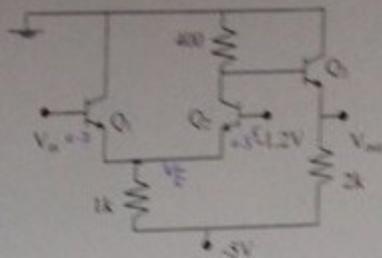Question III (10 points)

Consider the following circuit, if $V_{BEA}=0.7V$, $\beta=100$



a) If V_{in} =logic one

• Find V_{out}

~~$0.2 \text{ to } 7 \text{ V}_{out} = 0 \Rightarrow V_{out} = 0.8$~~
 ~~$-V_{in} + 0.7 + V_E = 0 \Rightarrow V_{in} = -0.95$~~

• Find I_{C1}

• Find I_{C2}

$= 0$

• Find I_{C3}

• Find power dissipation

$P = V_c I_c$

b) If V_{in} =logic zero

• Find V_{out}

• Find I_{C1}

$= 0$

• Find I_{C2}

• Find I_{C3}

• Find power dissipation

$P = V_c I_c$

EE Committee
 لجنة الهندسة الكهربائية

Q3 a) Q. on P2old

$V_c =$

(7)

$$V_c = -0 - \cancel{400} R_1 - 0.4 = -0.7$$

(2/10)



$$I_{B2} = (1 - 2\beta) I_{R1} = 0.2857 \text{ A}$$

$$I_{B1} = \frac{5 - 2.5}{R_2} \Rightarrow R_2 = 9.45 \text{ k}\Omega$$

b) $\beta I_{B1} \geq I_{R1}$

$$(50)(I_{B1}) \geq 100 \left(\frac{5 - 0.9}{2 \text{ k}} \right)$$

$$I_{B1} = 4.1 \text{ mA}$$

c)

$$I_A = \frac{5 - 2.3}{2 \text{ k}} = 1.35 \text{ A}$$


$$I = \beta I_A = 0.27 \text{ mA}$$

$$I_{E1} = 5 - I = 13.5 \text{ mA}$$

$$V_{CE} = 5 - 2 \text{ k} \cdot 13.5 \text{ mA} = 0.2 \text{ V}$$

$$V_{CE} = 5 - 2 \text{ k} \left(\frac{13.5 \text{ mA}}{\beta + 1} \right) = 0.2 \text{ V}$$


$$V_{CE} = 3 \text{ V}$$

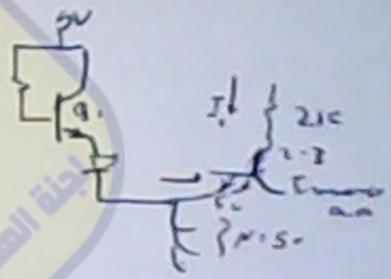

(i)

Solution to first exam:

Q1

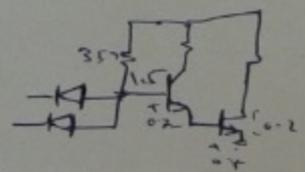

a) $V_{B1} = 0.7 + 0.8 = 1.5V$

b) $I_{B1} = \frac{5 - 1.5}{35k} = \dots$


$I_{C1} = \beta I_{B1} = 5\mu A$, $I_{C1}^{sat} = 10\mu A$, $I_{B2} = (\beta) I_{C1} = 5.1\mu A$
 Φ_1 Act

b) $\beta I_{B2} > \frac{5 - 2}{1k} + N \frac{5 - 0.9}{35k}$
 $N < 385.9$

c) $V_o = 5V$

d) $N M_0 = 0.7 - 0.2 = 0.5V$

$N M_1 = 5 - 0.8 = 4.2$

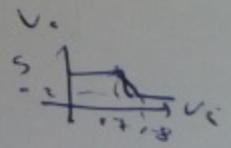

Q2) $I_{C2} = \frac{2\mu A}{\text{given}} + \frac{0.8}{2k} = 2.4\mu A$

a) $V_{C2} = 0.8 + 0.2 = 1V$

$I_{C2} = \frac{5 - 1}{2k} = 2\mu A$

5