

A

Jordan University of Science & Technology  
Electrical Engineering Department

First Examination  
Spring Semester 2003 / 2004

EE 332

Electrical Machines I

29.3.2004

**Problem 1**

The following test results are obtained for a 24 kVA , 2400 / 240 V , 50 Hz transformer:

No-Load Test 240 V , 5 A , 200 W

Short-Circuit Test 100 V , 10 A , 350 W

- Determine the approximate equivalent circuit parameters referred to the high voltage side. Draw the circuit and insert the parameters values. (8 marks)
- Calculate the output voltage when the transformer is connected to a 2.4 kV supply and supplies a load with rated current at a power factor of 0.8 lagging. (6 marks)
- What is the efficiency of the transformer and the voltage regulation at this load? (3 marks)
- Calculate the load current that will give maximum efficiency. What will be the maximum efficiency? (2 marks)
- The above transformer is to be used as a 2640 / 240 V autotransformer. Draw , *clearly* , the connection of the autotransformer. Calculate the supply current, the load current and the kVA rating of the autotransformer. (3 marks)

**Problem 2**

Three single phase , 110 kVA , 2200 / 440 V transformers are connected to form a three phase , 2200 / 440 V transformer bank. The equivalent impedance of each transformer referred to its low-voltage side is  $(0.048 + j 0.15) \Omega$  . The transformer is connected to a 3-phase source through 3-phase feeders, the impedance of each feeder being  $(0.5 + j1.5) \Omega$  . The transformer bank delivers full load at 440 V and 0.8 power factor lagging.

- Draw a schematic diagram showing the transformer connection. (2 marks)
- Determine the single-phase equivalent circuit. (3 marks)
- Determine the sending end line voltage of the 3-phase source. (3 marks)

Jordan University of Science & Technology  
Electrical Engineering Department

First Examination

EE 332

Electrical Machines I

27.7.2004

Q.1. A 6.6 kVA, 660/220 V, 50 Hz transformer gave the following test results :

Open Circuit test 660 V, 0.3 A, 40 W  
Short Circuit test 15 V, 30 A, 90 W

- Determine the equivalent circuit parameters referred to the high voltage side. Draw the equivalent circuit and insert the parameters.
- Determine the efficiency and voltage regulation when the transformer is supplying full-load at rated voltage and 0.8 power factor lagging.
- Repeat (b) for half full-load and 0.8 power factor leading.

(45%)

Q.2. A 12 kVA, 480/240 V, 50 Hz transformer has an efficiency of 95% when it delivers 9.6 kW at 0.8 power factor. The transformer is connected as an autotransformer to supply load to a 480 V circuit from a 720 V supply.

- Show a clear diagram of the autotransformer connection.
- Determine the maximum kVA the autotransformer can supply to the 480 V load.
- Determine the efficiency of the autotransformer for full-load at 0.8 power factor.

(25%)

Q.3. Three single phase, 15 kVA, 480 / 120 V transformers are connected to form a three phase, 480 / 208 V transformer bank. The equivalent impedance of each transformer referred to the high-voltage side is  $(1.5 + j3) \Omega$ . The transformer supplies a three-phase, 208 V, 32 kW, 0.8 power factor leading load.

- Draw a schematic diagram showing the transformer connection.
- Determine the transformer winding currents.
- Determine the primary voltage and voltage regulation.

(30%)

*Note : Write the Best answer in the Answer Box at the Bottom of the page.*

- A) A 150 kVA , 2400/240 V transformer has the following parameters :  $R_1 = 0.2 \Omega$  ,  $R_2 = 0.002 \Omega$  ,  $X_1 = 0.45 \Omega$  ,  $X_2 = 0.0045 \Omega$  ,  $R_{CH} = 10 k \Omega$  ,  $X_{MH} = 1.55 k \Omega$  . The secondary is delivering rated load current at rated voltage and 0.8 power factor lagging.
1. The voltage regulation is :  
a) 2.1%      b) 3.1%      c) 2.2%      d) 4.1%
  2. The efficiency at full load is :  
a) 97%      b) 97.5%      c) 98%      d) 98.2%
  3. The primary input voltage at full load is :  
a) 2400 V      b) 2453 V      c) 2380 V      d) 2498 V
  4. The maximum efficiency will occur at a percentage of full load equal to :  
a) 62%      b) 70%      c) 74%      d) 85%
  5. The load power factor angle that will give zero voltage regulation is :  
a) 24° lag      b) 24° lead      c) 37° lead      d) 37° lag
  6. The no-load current as a percentage of full-load current is :  
a) 2.1%      b) 3.5%      c) 2.6%      d) 4.1%
  7. The transformer is reconnected as a step-up 2400/2640 V autotransformer. The maximum kVA rating of the autotransformer is :  
a) 150      b) 1418      c) 1716      d) 1650
- B) Three of the transformers in (A) above are connected to form a 3-phase 2400/415 V transformer bank. The 3-phase transformer supplies a 3-phase 300 kVA , 415 V , 0.85 power factor lagging load.
8. The secondary line current is :  
a) 417 A      b) 355 A      c) 491 A      d) 722 A
  9. The primary phase current is :  
a) 72 A      b) 36 A      c) 49 A      d) 42 A
- C) A four-pole, separately excited dc generator has lap winding of 300 turns. The flux per pole is 0.025 Wb. The machine rotates at 1000 rpm. The armature resistance is 0.1  $\Omega$  and the rated current through the turn is 25 A.
10. The terminal voltage at full load is :  
a) 250 V      b) 247.5 V      c) 125 V      d) 240 V
  11. The output power of the machine at full load is :  
a) 24 kW      b) 25 kW      c) 12.5 kW      d) 6.25 kW
  12. The electromagnetic torque developed is :  
a) 229 Nm      b) 239 Nm      c) 60 Nm      d) 119 Nm

*Answers*

1	2	3	4	5	6	7	8	9	10	11	12

Electrical Engineering Department  
First Exam EE 332  
Electric Machines

Dr. Ahmad Harb

July 25, 2002

Q1:

- a) A single phase transformer (220 KVA, 11 / 2.2 KV) is to be used as an autotransformer. Draw the connection that will result in maximum KVA rating and calculate this KVA rating.
- b) What is the armature reaction effect? And how can you reduce that effect?

Q2: A single phase transformer (10 KVA, 2200/220 V, 60 Hz) has the following equivalent circuit parameters (in ohms):

$$Z_{eq, II} = 10.4 + j 31.3$$

$$R_{cII} = 48400$$

$$X_{mII} = 8980$$

Standard no-load and short-circuit tests are performed on this transformer. Determine the no-load as well as the short-circuit tests values (V, I, and P)

Q3: A dc machine (6 KW, 120 V, 1200 rpm) has the following magnetization characteristics at 1200 rpm.

$I_f$	0.0	0.1	0.2	0.3	0.4	0.5	0.6	0.8	1.0	1.2	(A)
$E_a$	5.0	20	40	60	79	93	102	114	120	125	(V)

The machine parameters are  $R_a = 0.2$  ohm,  $R_{fw} = 100$  ohm. The machine is driven at 1200 rpm and is separately excited. The field current is adjusted at  $I_f = 0.8$  A. A load resistance  $R_L = 2$  ohm is connected to the armature terminals.

- No armature reaction:

- (a) Determine the quantity  $K_a \phi$  for the machine.  
(b) Determine  $E_a$  and  $I_a$ .  
(c) Determine the torque T and load power  $P_L$ .

- Repeat the above three parts with the present of armature reaction 0.2 A

*With my best wishes for all of you*

Dr. Ahmad Harb

Jordan University of Science & Technology  
Electrical Engineering Department

First Examination

EE 332

Electrical Machines I

13.11.2002

Q.1. A 220 kVA, 11 kV / 2.2 kV, single phase transformer has the following parameters:

$$\begin{aligned} R_{HV} &= 1.3 \, \Omega & X_{HV} &= 4.5 \, \Omega \\ R_{LV} &= 0.05 \, \Omega & X_{LV} &= 0.16 \, \Omega \\ R_{C(LV)} &= 2.4 \, k\Omega & X_{m(LV)} &= 0.8 \, k\Omega \end{aligned}$$

- Draw the approximate equivalent circuit referred to the HV side and show the parameter values.
- Determine the no-load current in amperes and as a percentage of rated current.
- If the low-voltage winding terminals are shorted, determine:
  - The supply voltage required to pass rated current through the shorted winding.
  - The losses in the transformer.
- The HV winding of the transformer is connected to the 11 kV supply and a load,  $Z_L = 15 \angle -90^\circ \, \Omega$  is connected to the low-voltage winding. Determine:
  - Load voltage.
  - Voltage regulation.

(50%)

Q.2. A six-pole, 1500 rpm, dc generator has 48 armature slots with 6 conductors per slot. The flux per pole is 20 mWb and each armature conductor has a maximum current carrying capacity of 40 A.

- Calculate the terminal voltage, armature current and power rating for a lap winding.
- Repeat part (a) for a wave winding.

(25%)

Q.3. Three, single phase, 15 kVA, 480 / 120 V transformers are connected to form a three phase, 480 / 208 V transformer bank. The equivalent impedance of each transformer referred to the high-voltage side is  $(1 + j2) \, \Omega$ . The transformer supplies a three-phase, 208 V, 32 kW, 0.8 power factor leading load.

- Draw a schematic diagram showing the transformer connection.
- Determine the transformer winding currents and the primary input current.
- Determine the primary voltage and voltage regulation.

(25%)