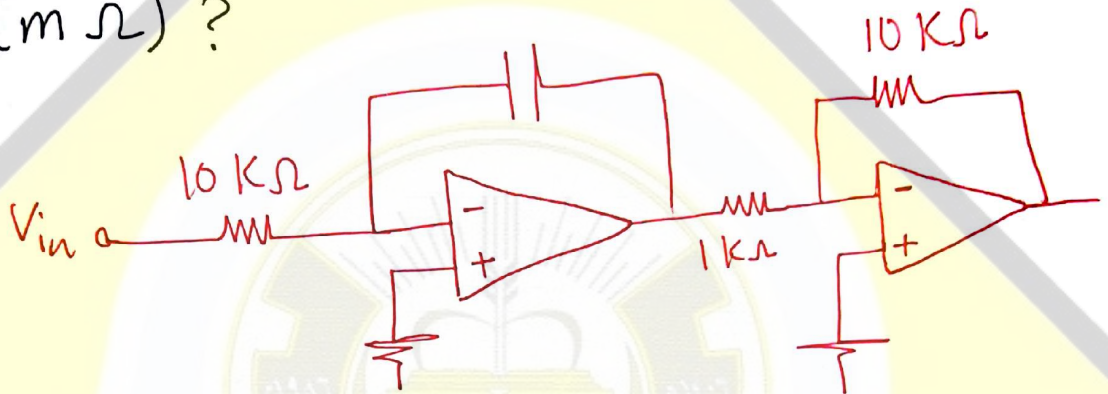


Q1 (multiple choice).

1- Sensor resolution when the offset  $V_{ab} = 3V$  is (m $\Omega$ )?



-Fig. 2-

2- 5 bit ADC with  $V_{ref} = 10V$ ,  $V_{in} = 0V$ , then the digital value of the input is ?

3- if  $C = 10 \mu F$ , initially uncharged and  $V_{in} = 10V$ , then  $V_{out}$  after 2 ms will be in fig 2 ?

4- One of the following is not a systematic error?

. nearby short circuit : القرب من الدارة

Q2 (essay).

A meter reads current through  $R$  of 30 mA with accuracy of  $\pm 1.5\%$  at full scale of 150 mA,  $R$  is measured as  $45.05 \Omega$ . Consider only s.f.

A- Find the voltage across  $R$  with worst case uncertainty expressed in  $V$ .


B- Use RMS representation to find the percentage uncertainty in  $V$  across  $R$ .

Q2 (essay).

Measurement of temperature, using a sensor that outputs  $10 \text{ mV}/^\circ\text{C}$ , using 4 bit ADC with 5V reference in the circuit.

A- What is the maximum temperature the circuit is designed to measure?

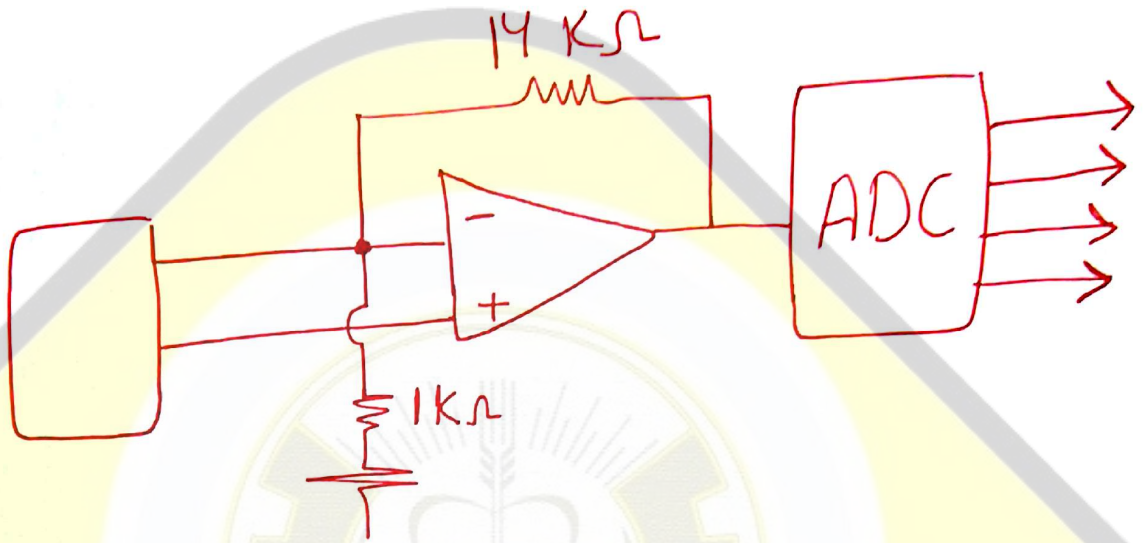B. if the output is 1010, what is the temp. range at this reading?



Q4 (essay).

Sensor resistance varies linearly from  $5 \rightarrow 15$  ( $\text{k}\Omega$ ) as a variable change from minimum to maximum value for this sensor.

A. design signal condition system that provides an output voltage varying linearly from  $-5 \rightarrow 5\text{ V}$  as sensor changes from min. to max. Use non-inverting and differential amplifier.

- don't use follower - , use  $1\text{ k}\Omega$  value for all fixed  $R$  in design.

B - Enter the output obtained from the Previous circuit to a hysteresis Comparator that will go high (5V) when the  $R_2$  is greater than  $10\text{ k}\Omega \pm 1\%$ .

C - Calculate the Power dissipated in the sensor . when the output is 0V . (bonus) .

EE committee  
لجنة الهندسة الكهربائية