Jordan University of Science & Technology Electrical Engineering Department Second Examination

EE 332

Electrical Machines I

15.8.2004

Name:		Univ.#:			
Note: Write the Bes	b) 89.7% c) 88.2% d) 91.3% rque of the motor is: b) 602 Nm c) 687 Nm d) 612 Nm				
A 3-phase, 60 Hz, 4 po 120 kW the core loss is kW.	ole, induction motor s 1.7 kW, the mech	runs at 1728 rpm. The panical loss is 2.7 kW and	power crossing the air gap is the stator copper loss is 3.5		
1. The efficiency of the range a) 87.2%		c) 88.2%	d) 91.3%		
2. The output torque of ta) 541 Nm		c) 687 Nm	d) 612 Nm		
$R_2 = 0.21 \Omega$, $X_m = 20 \Omega$	z, 4 pole, Y-connect $P_r = 1.6 \text{ kW}$. The	ted induction motor has R motor is operated at 1455	$x_1 = 0.25 \Omega$, $X_1 = X_2 = 0.6 \Omega$, rpm.		
3. The input power is: a) 19.4 kW	b) 23.1 kW	c) 31.6 kW	d) 20.5 kW		
4. The output horse power a) 37.2 hp	er is: b) 23.4 hp	c) 24.5 hp	d) 40.8 hp		
5. The slip at maximum a) 0.172	torque is: b) 0.124	c) 0.214	d) 0.157		
6. The maximum develop a) 219.6 Nm	ped torque is: b) 349.4 Nm	c) 329.5 Nm	d) None of these		
rotates at 1500 rpm. Ra	$_{1}=0.5 \Omega.$	ich requires a constant to	rque of 300 Nm. The motor		
7. The armature current (a) 78.6 A	l _a is: b) 62.8 A	c) 56.5 A	d) 84.5 A		
If the shunt field flux of		reduced by 10% then:			
8. The new armature cur a) 69.1 A	b) 62.8 A	c) 93.9 A	d) 88.5 A		
9. The speed of the moto a) 1653 rpm	or is: b) 1456 rpm	c) 1667 rpm	d) 1310 rpm		
A 220 V, 12 hp, dc ser The armature reaction 10. The speed (rpm) of t	at 40 A reduces the	A and rotates at 1200 rpn flux by 5%. If the motor	1. $R_n = 0.25 \Omega$, $R_s = 0.1 \Omega$. draws 20 A, then:		
a) 2357		c) 2482	d) 1179		
11. The developed torque a) 16.4 Nm		c) 32.8 Nm	d) 34.5 Nm		

A	n	C	w	P	r'S
7 7	11	J	11	•	1 2

1	2	3	4	5	6	7	8	9	10	11