

Mid Examination

EE 346

Introduction to Microcontrollers Lab


30.11.2010

12/22
30


Q1) a. Implement the following Boolean expressions using the given gates. Construct a circuit diagram and a pin out diagram on the chips shown below. Show your connections in details $z = (\bar{x}y + xy)$

1. $E = X'YZ + XY'Z$. Chips needed are: 7404(hex invertir), 7408(quad 2 input AND and gate) and 7432(quad 2 input OR gate)

Circuit diagram:

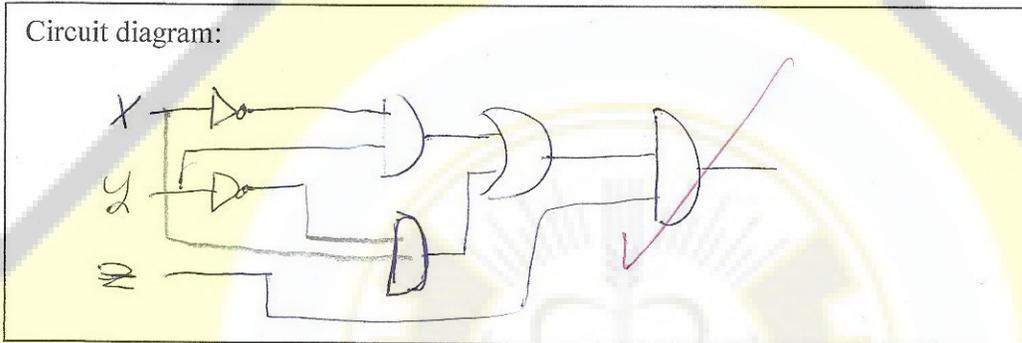


Pin out diagram:

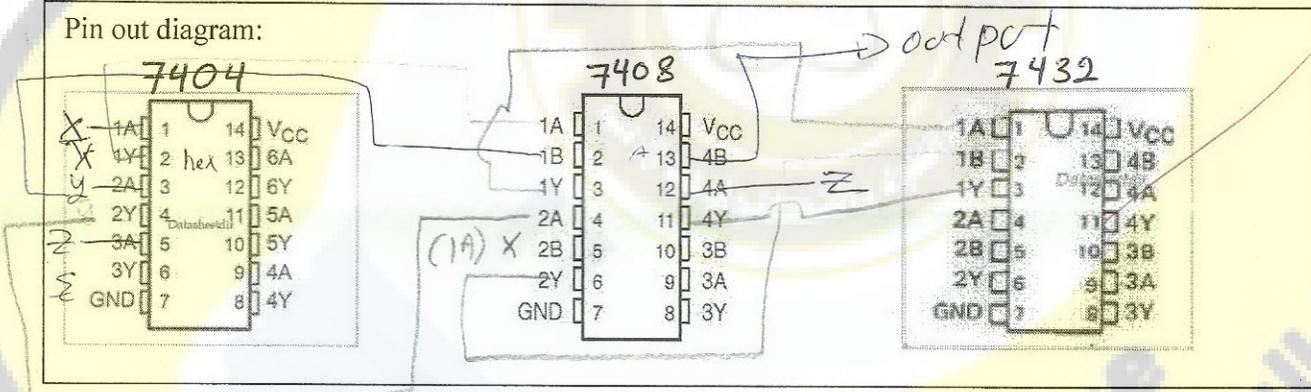


2. $D = X \oplus Y \oplus Z$. Chip needed 7486 (Quad 2 input XOR gate)

Circuit diagram:

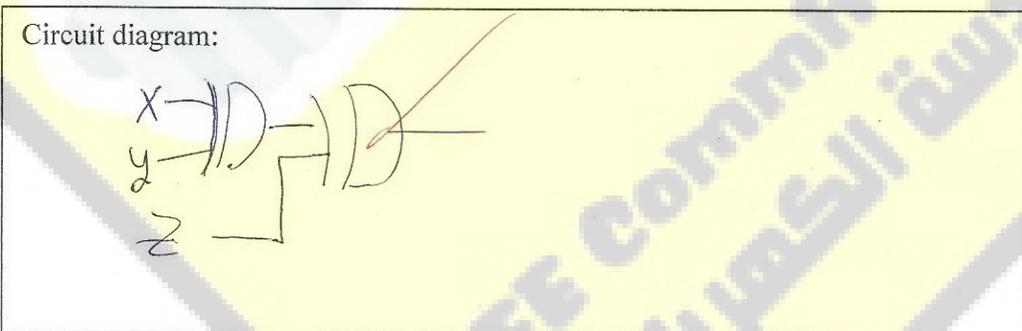

Pin out diagram:

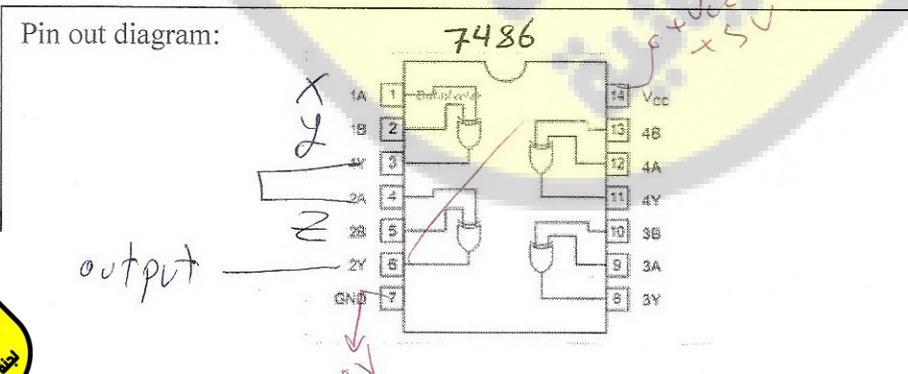

Q1. b. Implement the following 4- Boolean expressions using 3-half adders shown below.

$xy\bar{z}$
 $+ z(A+B)$
 $xy(z+a)$


$$D = X \oplus Y \oplus Z$$

$$E = X'YZ + XY'Z$$

$$F = XYZ' + (X + Y)Z$$

$$G = XYZ$$

$xy\bar{z} + yz$
 $xy(z+a)$

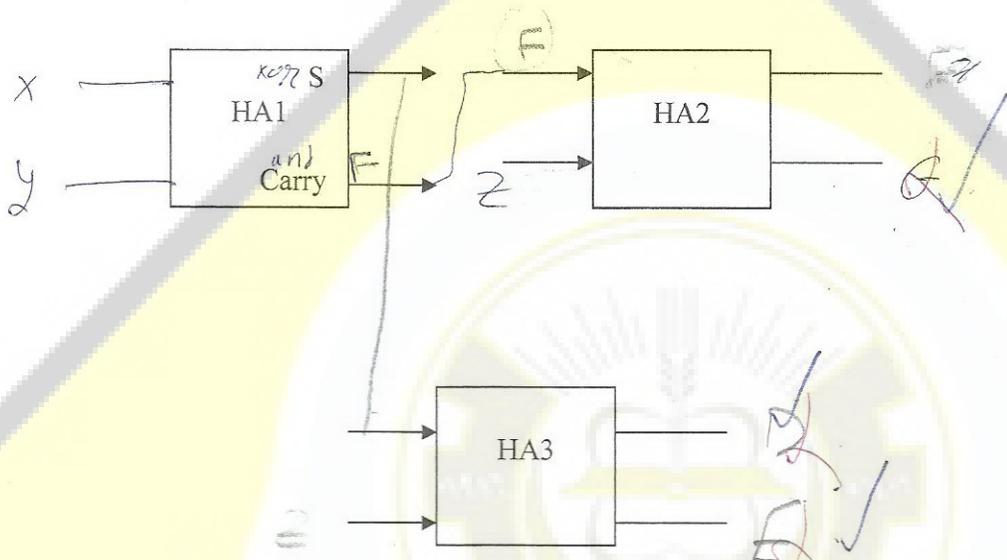



0

4



Q2. Implement the function in the truth table (keep the use of such gates to a minimum.)

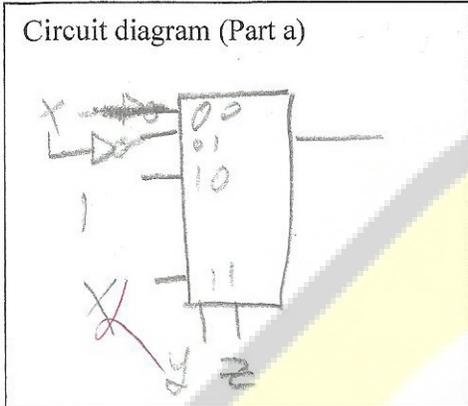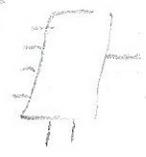a. Using 4*1 MUX (Use chip 74153 and any additional gates to construct your circuit)




X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Handwritten notes: $X \bar{Y} Z$, $X \bar{Y} \bar{Z}$, $\bar{X} Y Z$, $\bar{X} Y \bar{Z}$

Handwritten notes: $0 \bar{0} 0$, $0 \bar{0} 1$, $0 \bar{1} 1$


Handwritten notes: 4×2

Pin out diagram (Part a)

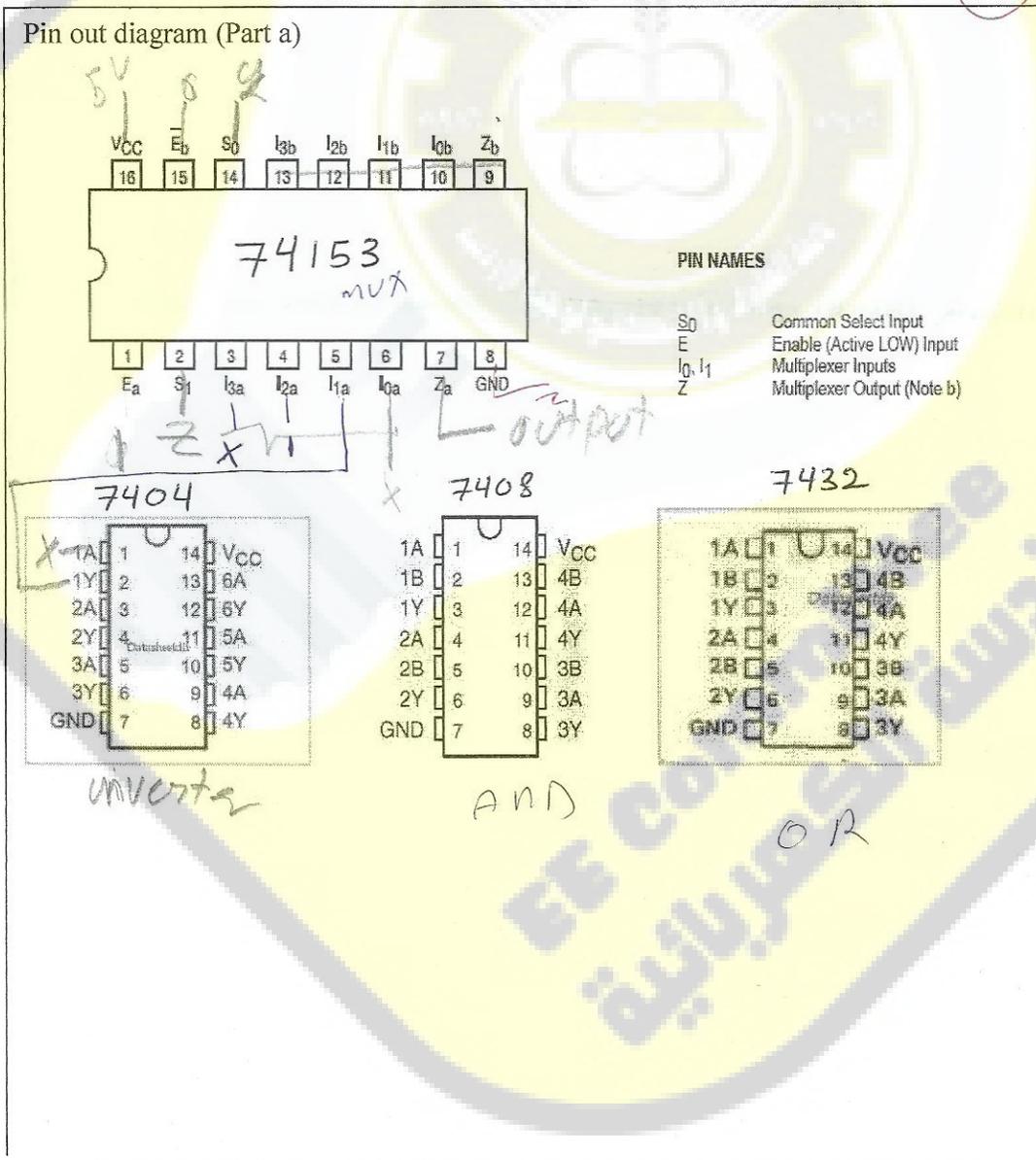


Q2. b. Using 3x8 Decoder (Use chip 74138 and any additional gates to construct your circuit)

Circuit diagram (Part b)

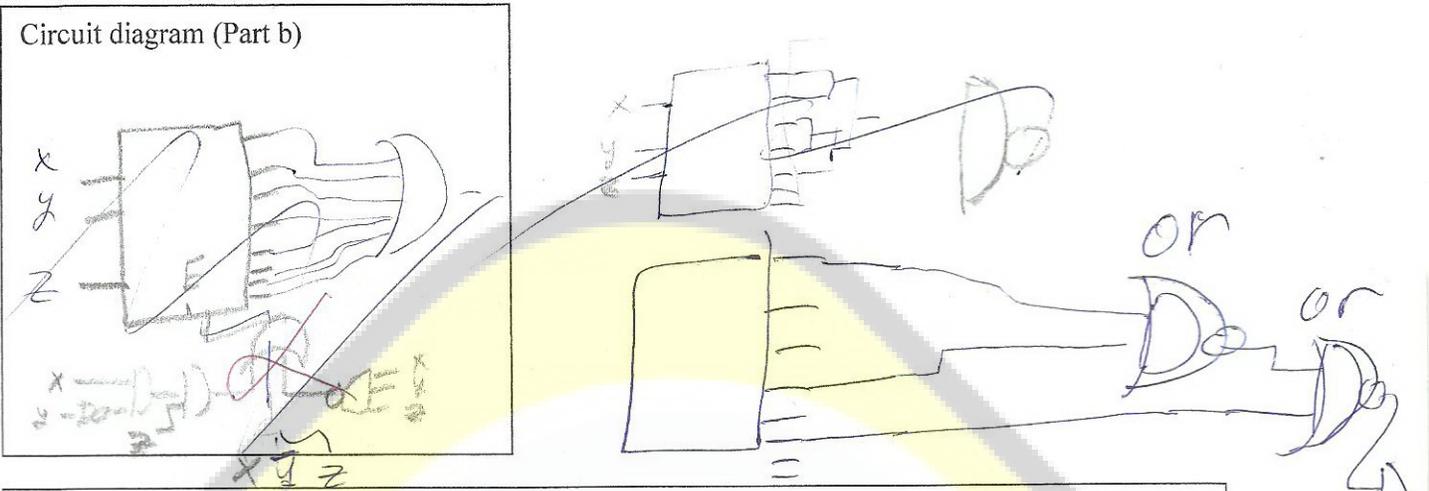

Pin out Diagram (Part b)

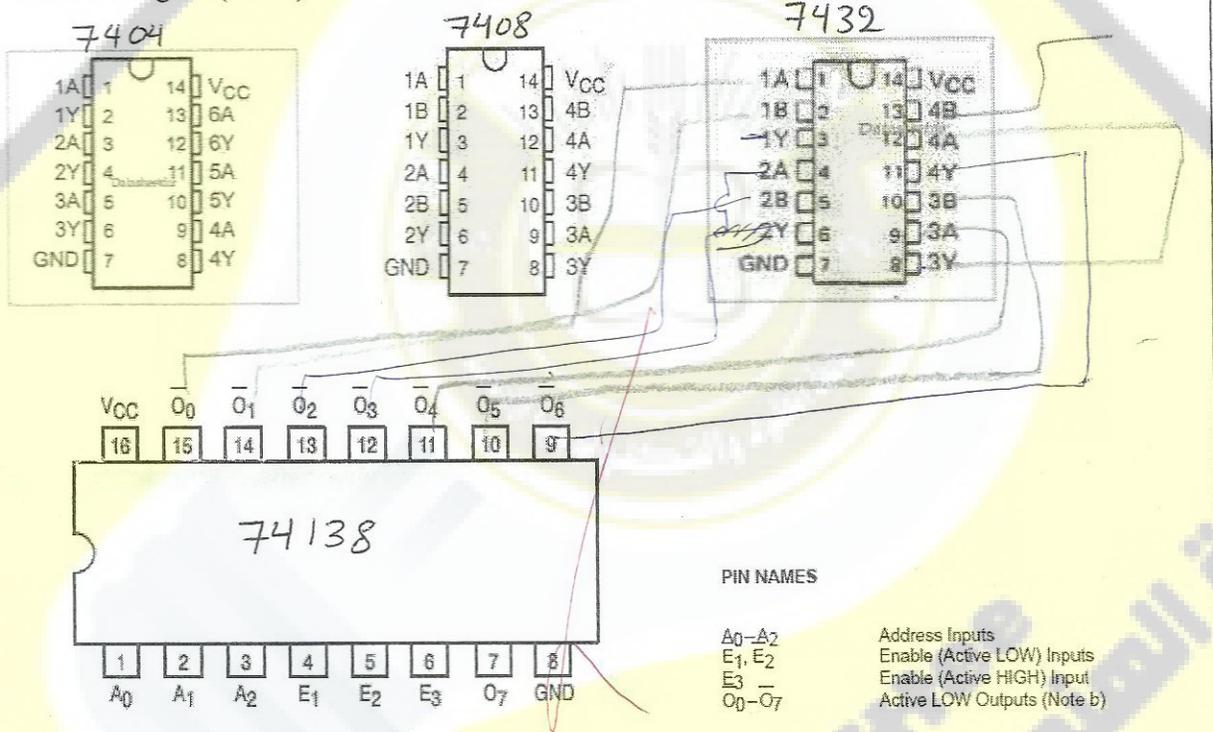



$$\frac{A \cdot B}{A + B}$$

(0)



0-4

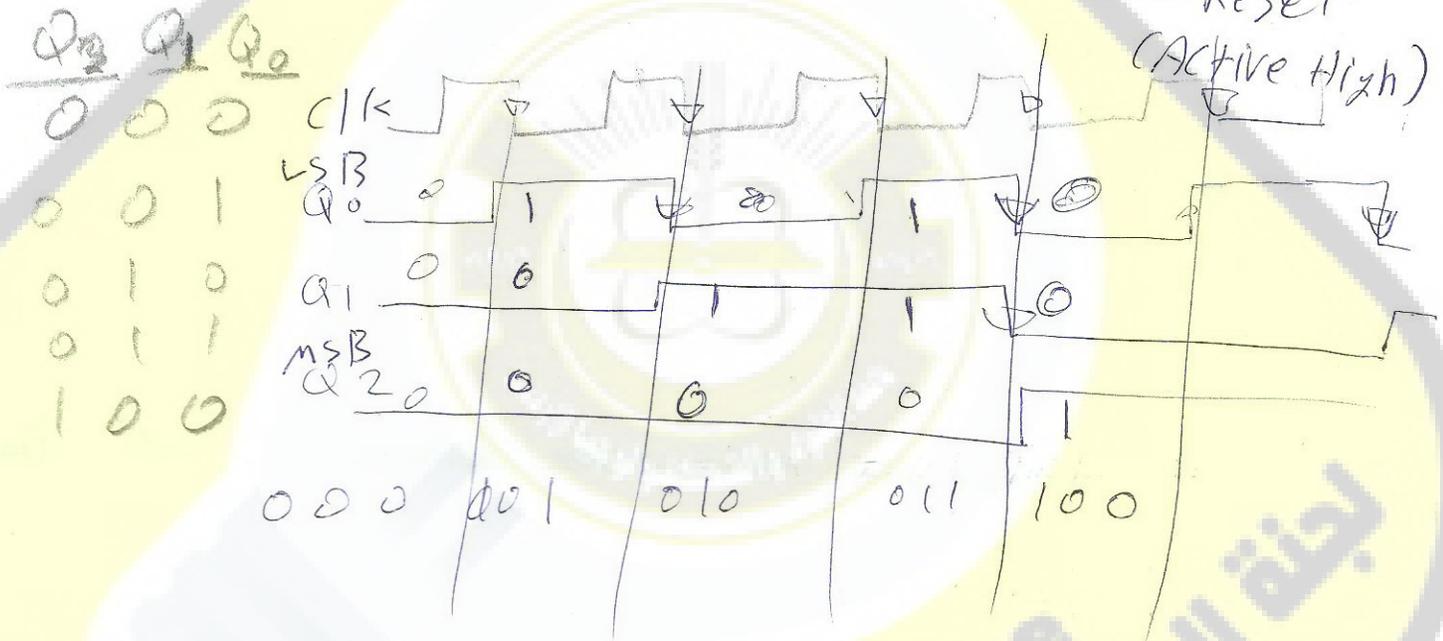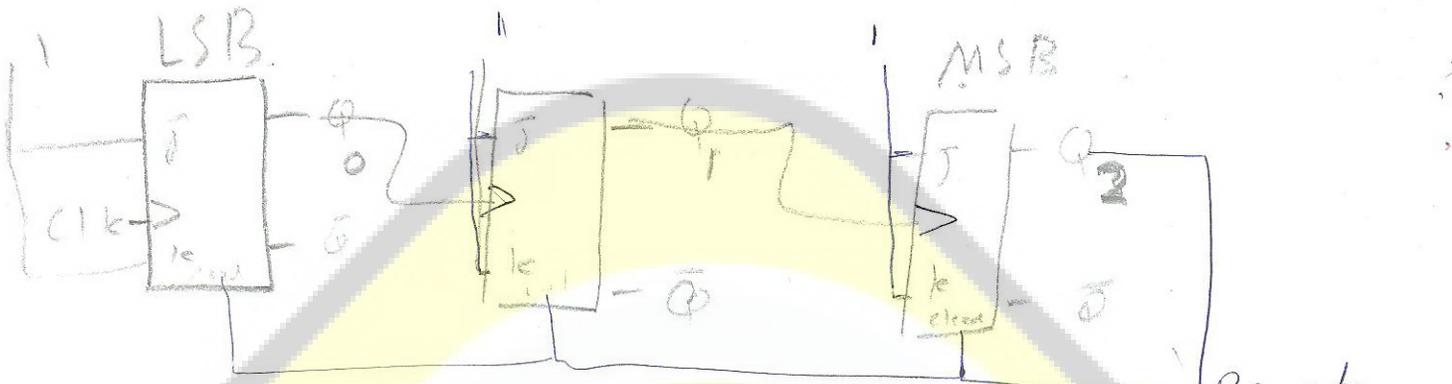Q3. Design a Mod-5 ripple counter using JK flip flops. (Show your circuit diagram in details)



Good Luck

