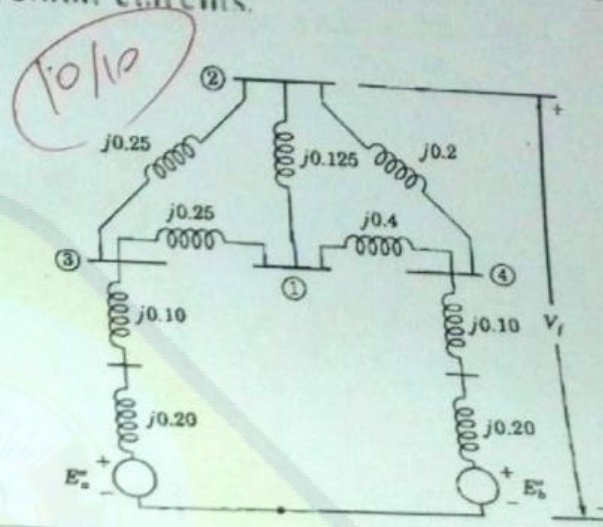


A three-phase fault occurs at bus (2) of the network of Fig. 10.5. Determine the initial symmetrical rms current (that is, the subtransient current) in the fault; the voltages at buses (1), (3), and (4) during the fault; the current flow in the line from bus (3) to bus (1); and the current contributions to the fault from lines (3) - (2), (1) - (2), and (4) - (2). Take the prefault voltage V_f at bus (2) equal to $1.0 \angle 0^\circ$ per unit and neglect all prefault currents.

$$Z_{bus} = \begin{matrix} & \textcircled{1} & \textcircled{2} & \textcircled{3} & \textcircled{4} \\ \begin{matrix} \textcircled{1} \\ \textcircled{2} \\ \textcircled{3} \\ \textcircled{4} \end{matrix} & \begin{bmatrix} j0.2436 & j0.1938 & j0.1544 & j0.1456 \\ j0.1938 & j0.2295 & j0.1494 & j0.1506 \\ j0.1544 & j0.1494 & j0.1954 & j0.1046 \\ j0.1456 & j0.1506 & j0.1046 & j0.1954 \end{bmatrix} \end{matrix}$$


$$(Z_{22} - 1) = 0$$

Fault @ bus (2)

$$i_f'' = \frac{Z_{22}^{-1} V_f}{Z_{22}} = -j4.35729 \text{ pu}$$

$$-V_3 + Z_{32} i_f'' + V_f = 0$$

~~$$V_3 = V_f - Z_{32} i_f''$$~~

$$V_3 = 0.3490 \text{ pu}$$




$$-V_1 + 1 - i_f'' Z_{12} = 0$$

~~$$V_1 = 1 - i_f'' (Z_{12})$$~~

$$V_1 = 0.1556 \text{ pu}$$


$$-V_4 + 1 - i_f'' Z_{42} = 0$$

$$V_4 = 0.34379 \text{ pu}$$

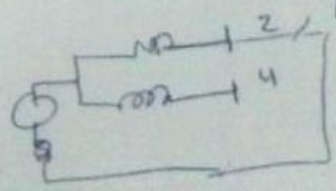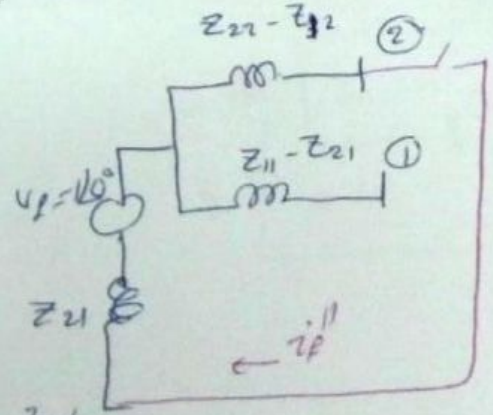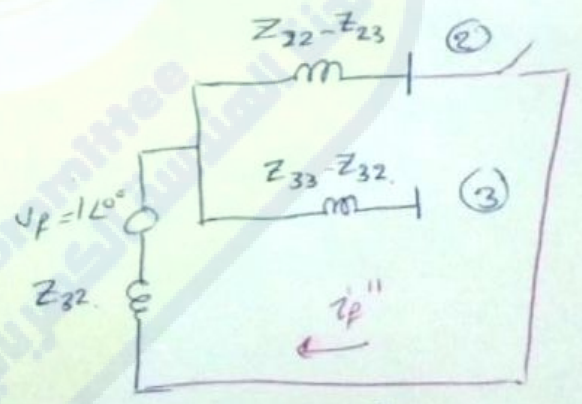

ANS ←



A five-bus network has generators at buses ① and ③ rated 270 and 225 MVA, respectively. The generator subtransient reactances plus the reactances of the transformers connecting them to the buses are each 0.30 per unit on the generator rating as base. The turns ratios of the transformers are such that the voltage base in each generator circuit is equal to the voltage rating of the generator. Line impedances in per unit on a 100-MVA system base are shown in Fig. 10.8. All resistances are neglected. Using the bus impedance matrix for the network which includes the generator and transformer reactances, find the

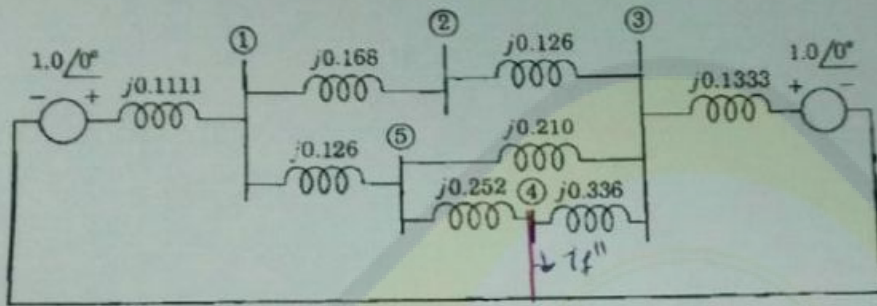

$$Z_{bus} = \begin{matrix} & \text{①} & \text{②} & \text{③} & \text{④} & \text{⑤} \\ \begin{matrix} \text{①} \\ \text{②} \\ \text{③} \\ \text{④} \\ \text{⑤} \end{matrix} & \begin{bmatrix} j0.0793 & j0.0558 & j0.0382 & j0.0511 & j0.0608 \\ j0.0558 & j0.1338 & j0.0664 & j0.0630 & j0.0605 \\ j0.0382 & j0.0664 & j0.0875 & j0.0720 & j0.0603 \\ j0.0511 & j0.0630 & j0.0720 & j0.2321 & j0.1002 \\ j0.0608 & j0.0605 & j0.0603 & j0.1002 & j0.1301 \end{bmatrix} \end{matrix}$$

10/10

$Z_{44} - Z_{34}$ faulted bus

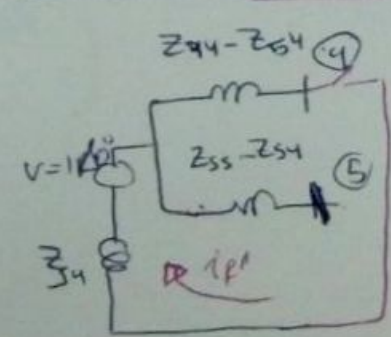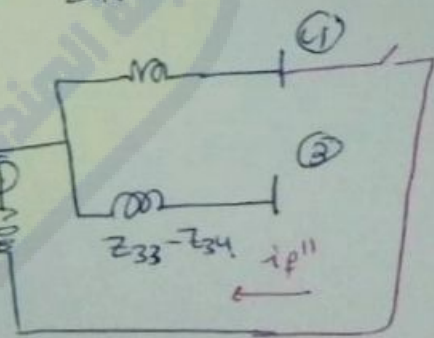

$$i_f'' = \frac{V_F}{Z_{44}} = -j4.308 \text{ pu.}$$

$$V_3 = 1 - i_f'' Z_{34}$$

$$V_3 = 0.6899 \text{ pu}$$

$$V_5 = 1 - i_f'' Z_{54}$$

$$= 0.56829 \text{ pu.}$$


$$I_{54} = \frac{V_5 - 0}{j0.252} = -j2.251 \text{ pu.}$$

$$I_{34} = \frac{0.6899 - 0}{j0.336} = -j2.0527 \text{ pu.}$$

$$I_{54} + I_{34} = -j4.308 \text{ pu}$$

Derive the sequence components and draw the sequence circuits of a Y grounded synchronous machine

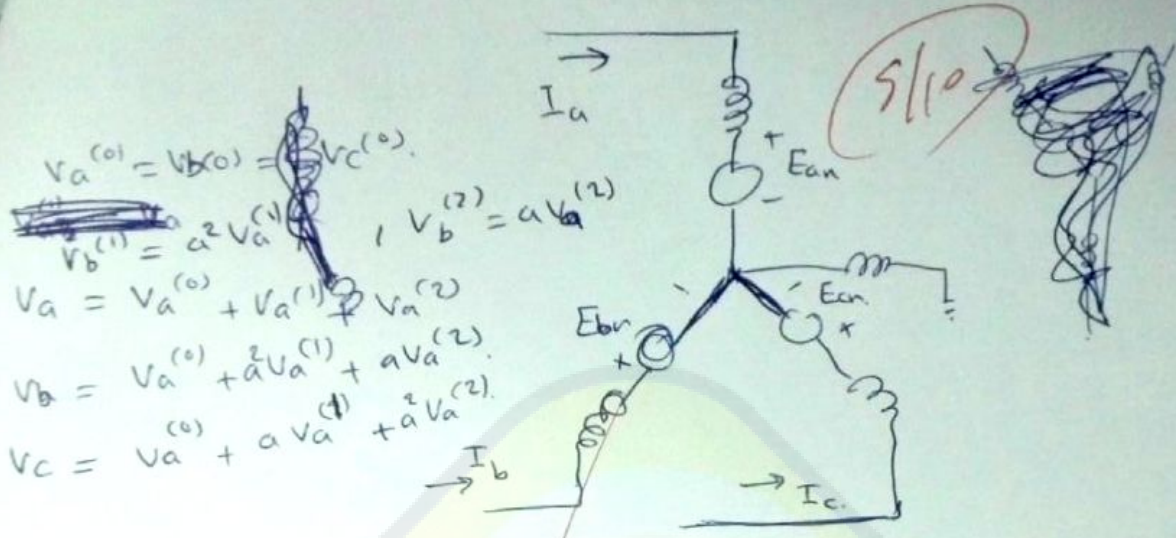Derive the sequence components and draw the sequence circuits of a Δ -Y grounded Transformer.



$$V_a^{(0)} = V_b^{(0)} = V_c^{(0)}$$

$$V_b^{(1)} = a^2 V_a^{(1)}, \quad V_b^{(2)} = a V_a^{(2)}$$

$$V_a = V_a^{(0)} + V_a^{(1)} + V_a^{(2)}$$

$$V_b = V_a^{(0)} + a^2 V_a^{(1)} + a V_a^{(2)}$$

$$V_c = V_a^{(0)} + a V_a^{(1)} + a^2 V_a^{(2)}$$

$$V_{abc} = A V_{012}$$

$$\begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} = A \begin{bmatrix} V_{ab}^{(0)} \\ V_{ab}^{(1)} \\ V_{ab}^{(2)} \end{bmatrix}$$

$$A = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix}$$

$$A^{-1} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a & a^2 \\ 1 & a^2 & a \end{bmatrix}$$

$$V_{ab} = V_a - V_b = [V_a^{(0)} + V_a^{(1)} + V_a^{(2)}] - [V_b^{(0)} + V_b^{(1)} + V_b^{(2)}]$$

same

$$V_{bc} = V_b - V_c = \text{like previous} = [V_b^{(0)} + V_b^{(1)} + V_b^{(2)}] - [V_c^{(0)} + V_c^{(1)} + V_c^{(2)}]$$

$$V_{ca} = V_c - V_a = [V_c^{(0)} + V_c^{(1)} + V_c^{(2)}] - [V_a^{(0)} + V_a^{(1)} + V_a^{(2)}]$$

then

$$V_a^{(1)} = \frac{1}{\sqrt{3}} V_{an} \angle 30^\circ, \quad V_a^{(2)} = V_{an} \angle -30^\circ$$

$$V_b^{(1)} = \frac{1}{\sqrt{3}} a^2 V_{an} \angle 30^\circ$$






In Delta.

$$i_a = (i_b + i_c)$$

~~$$V_a = V_{an} + \dots$$~~

ΔY transformer.

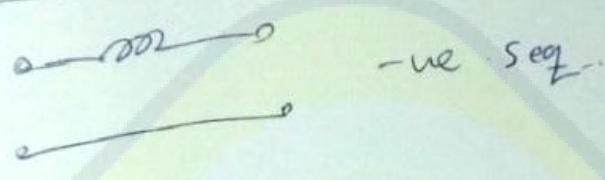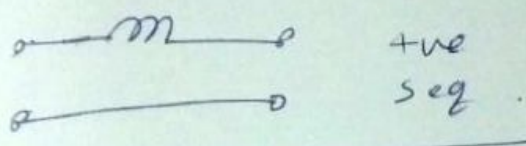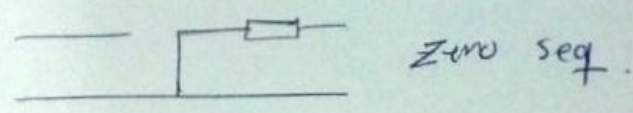

if there is any source E_{an} we put it.

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = -[R + j\omega L_s + M_s] \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} + j\omega M_s \begin{bmatrix} 1 & 1 & 1 \\ 1 & 1 & 1 \\ 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} + \begin{bmatrix} E_{an} \\ E_{bn} \\ E_{cn} \end{bmatrix}$$

using A^{-1}

$$\begin{bmatrix} V_{ab}^{(0)} \\ V_{ab}^{(1)} \\ V_{ab}^{(2)} \end{bmatrix} = -[R + j\omega(L_s + M_s)] \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} + j\omega M_s \begin{bmatrix} 3 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_a^{(0)} \\ I_a^{(1)} \\ I_a^{(2)} \end{bmatrix} + \begin{bmatrix} 0 \\ E_{bn} \\ 0 \end{bmatrix}$$

$$V_{ab}^{(0)} = -[R + j\omega(L_s + M_s)] I_a^{(0)} + 3j\omega M_s I_a^{(0)} + 0$$

$$V_{ab}^{(1)} = -R_a I_a^{(1)} + 2j\omega M_s I_a^{(1)} + j\omega L_s I_a^{(1)} + E_{bn}$$

$$V_{ab}^{(2)} = -R_a I_a^{(2)} + j\omega(L_s + M_s) I_a^{(2)} + E_{bn}$$